



KTU **NOTES**

The learning companion.

**KTU STUDY MATERIALS | SYLLABUS | LIVE
NOTIFICATIONS | SOLVED QUESTION PAPERS**

Module : 3

Phasors

4 types of phasors are:

1) Rectangular form

2) Trigonometric form


3) Exponential form

4) Polar form

$j = \sqrt{-1}$, j is an operator. It is used to express the 90° operation in counter clockwise direction.


1) Rectangular form

$$\cdot V = x + jy$$

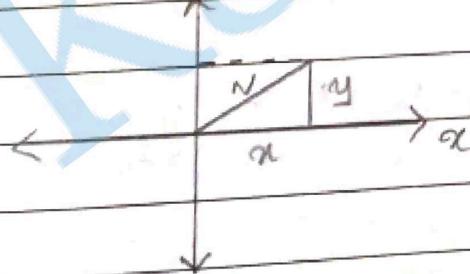

$$\{ j = i = \sqrt{-1} \}$$

2) Trigonometric form

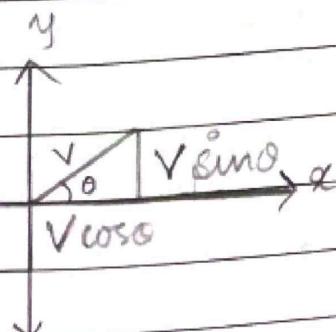

$$V = V(\cos\theta + j\sin\theta)$$

→ Exponential Form ($e^{j\theta}$)

$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$e^{-j\theta} = \cos\theta - j\sin\theta$$

$$V = V e^{-j\theta}$$

→ Polar Form

$$V = V \angle \theta$$

{ θ - angle of}

•) Addition & Subtraction

(most suitable for rectangular form)

$$V_1 = x_1 + jy_1$$

$$V_2 = x_2 + jy_2$$

$$V_1 + V_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$V_1 - V_2 = (x_1 - x_2) + j(y_1 - y_2)$$


•) Multiplication and division (polar form)

$$V_1 = V_1 \angle \theta_1$$

$$V_2 = V_2 \angle \theta_2$$

$$V_1 \cdot V_2 = V_1 V_2 \angle (\theta_1 + \theta_2)$$
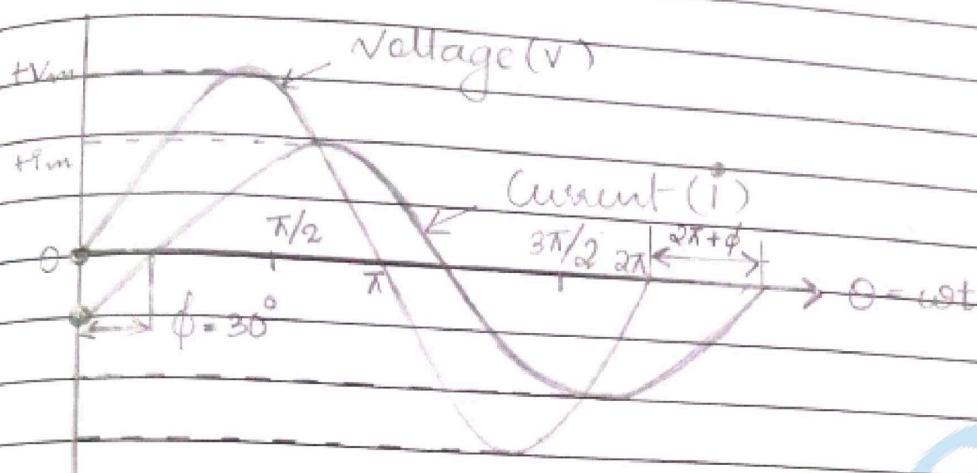
$$\frac{V_1}{V_2} = \frac{V_1}{V_2} \angle (\theta_1 - \theta_2)$$




{out of phase}

$$v = V_m \sin(\omega t)$$

reference wave

$$i = I_m (\omega t - \phi)$$

lagging by ϕ degree

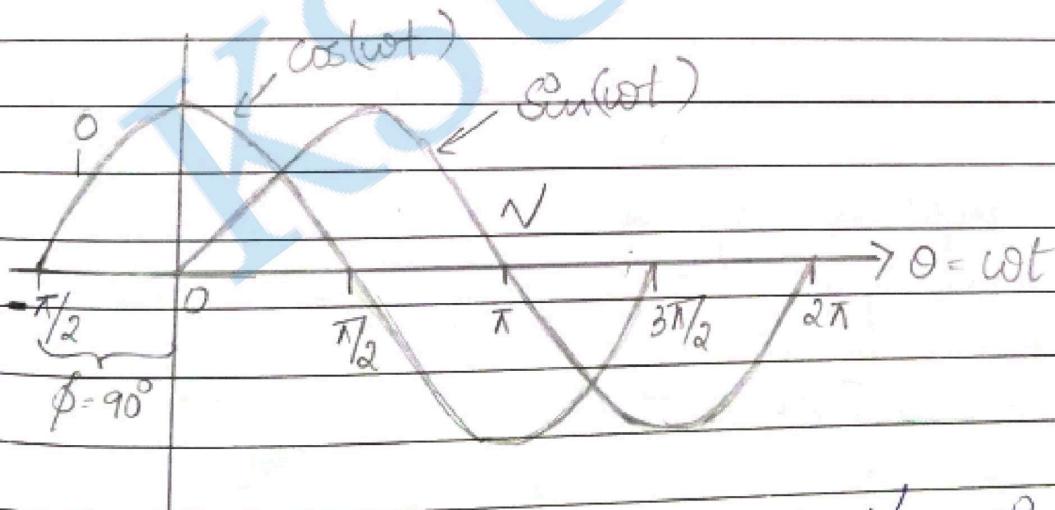

$$v = V_m \sin(\omega t)$$

reference wave

$$i = I_m \sin(\omega t + \phi)$$

leading wave

leading by ϕ degree

AC Circuit with resistance only

$$v = V_m \sin \omega t$$

$$v = I R$$

$$V_m \sin(\omega t) = I R$$

$$I = \frac{V_m \sin(\omega t)}{R}$$

$$\therefore I_m = \frac{V_m}{R}$$

$$(I = I_m \sin(\omega t))$$

Instantaneous power,

$$P = vi$$

$$= V_m I_m \sin^2(\omega t)$$

$$= V_m I_m (1 - \cos 2\omega t)$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2}$$

$$P = V_m I_m \sin^2 \omega t$$

$$I = I_m \sin \omega t$$


Power consist of a constant part:

$$\Rightarrow \frac{V_m I_m}{2}$$

and a fluctuating part:

$$\Rightarrow \frac{V_m I_m \cos(2\omega t)}{2}$$

frequency is double that of voltage

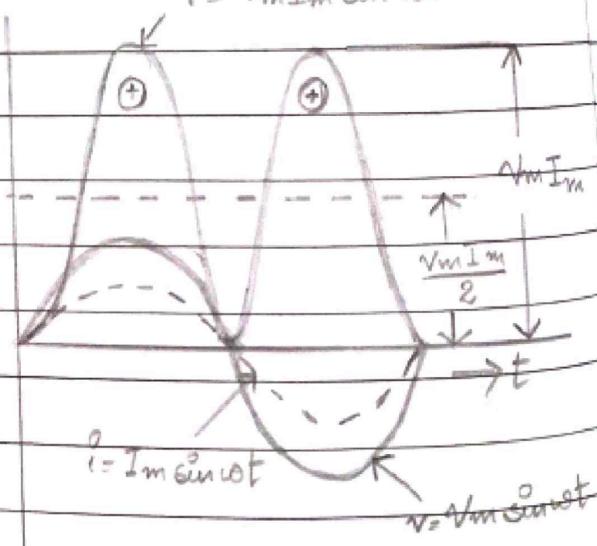

ind current waves.

Hence, power for the whole cycle is

$$P = \frac{V_m I_m}{2} = \frac{V_m \times I_m}{\sqrt{2} \sqrt{2}}$$

or $P = V \times I \text{ (Wt)}$

where,

V = rms value of applied voltage.

I = rms value of the current.

AC through Pure Inductive Circuit

$$v = L \frac{di}{dt}$$

Now, $v = V_m \sin(\omega t)$

$$\therefore V_m \sin(\omega t) = L \frac{di}{dt}$$

$$\therefore di = \frac{V_m}{L} \sin(\omega t) dt$$


Integrating both sides
we get,

$$i = \frac{V_m}{L} \int \sin(\omega t) dt$$

$$= \frac{V_m}{L} \cos \omega t$$

$$\therefore i = \frac{V_m}{L} \sin \left(\omega t - \frac{\pi}{2} \right)$$
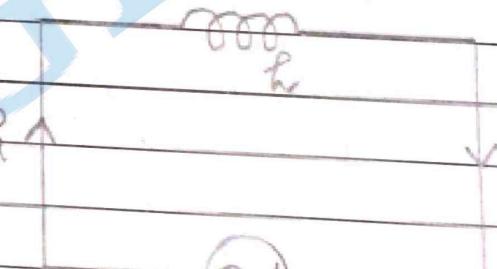
$$= \frac{V_m}{L} \sin \left(\omega t - \frac{\pi}{2} \right)$$




$$v = V_m \sin(\omega t)$$



Max value of i is $I_m = \frac{V_m}{jR}$ (when)

$\sin(\omega t - \frac{\pi}{2})$ is unity)
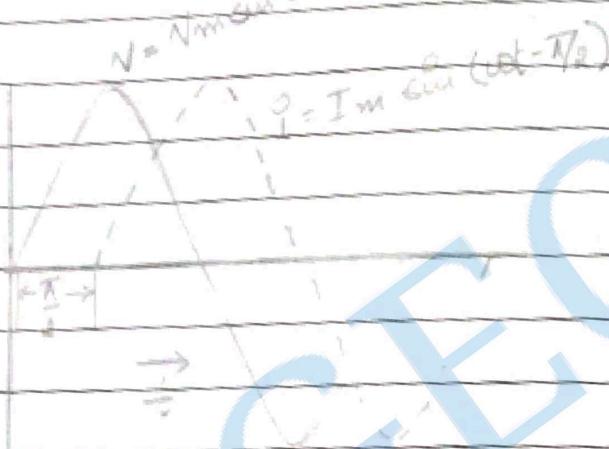
$$i = I_m \sin(\omega t - \frac{\pi}{2})$$



Power

$$\text{Instantaneous power} = Vi = V_m I_m \sin \omega t \sin(\omega t - \frac{\pi}{2})$$


$$= V_m I_m \sin(\omega t) \cos(\omega t)$$

$$= \frac{V_m I_m}{2} \sin(2\omega t)$$

$$\text{Power for whole cycle is } P = \frac{V_m I_m}{2} \int_0^{2\pi} \sin^2 \omega t dt$$

$$= 0$$

Power wave

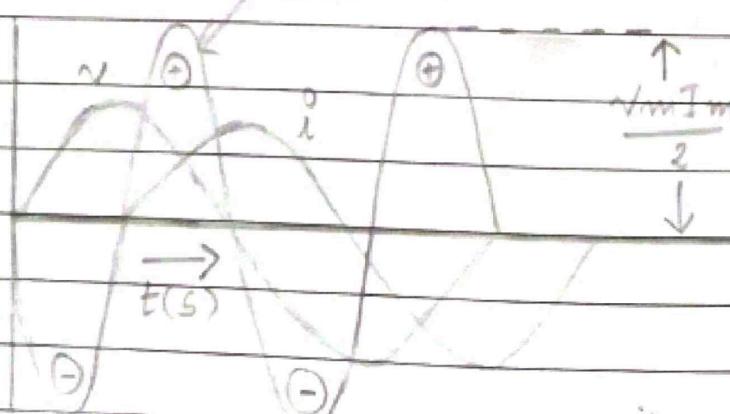

AC through Pure Capacitive Circuit

- v = p.d developed between plates at any instant.
- q = charge on plates at that instant

$$q = Cv \quad \{ \text{where } C \text{ is } \}$$

[the capacitance]

$$= C V_m \sin(\omega t) \quad \{ \text{sub } v = V_m \sin(\omega t) \}$$

current i is given by the rate of flow of charge.

$$\therefore i = \frac{dq}{dt}$$

$$= \frac{d(C V_m \sin \omega t)}{dt}$$

$$= C V_m \omega \cos \omega t \text{ or } I$$



$$I = \frac{V_m \sin(\omega t + \frac{\pi}{2})}{1/C\omega}$$

$$I_m = \frac{V_m}{1/C\omega} = \frac{V_m}{X_C}$$



$$q = I_m \sin(\omega t + \frac{\pi}{2})$$

$$P = VI$$
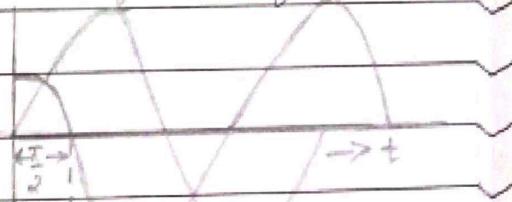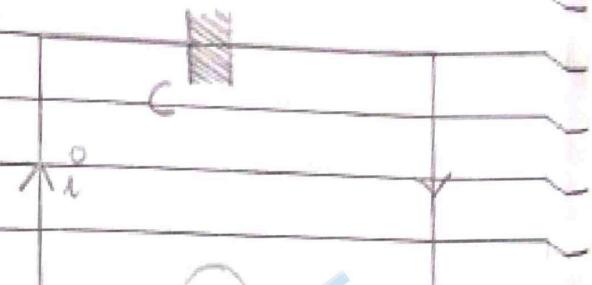
$$= V_m \sin(\omega t) \cdot I_m \sin(\omega t + \frac{\pi}{2})$$



$$q = I_m \sin(\omega t + \pi/2)$$

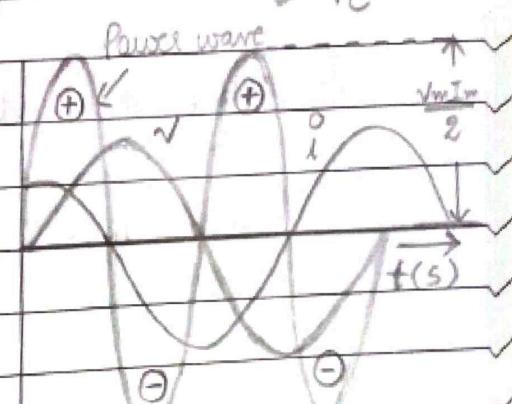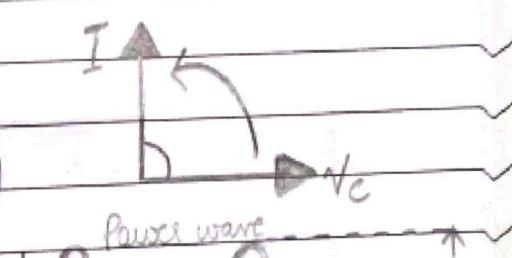

$$P = VI$$

$$V_m I_m \sin \omega t \cos \omega t$$

$$= V_m I_m \sin^2 \omega t$$

Power for the whole cycle

$$= V_m I_m \int_0^{2\pi} \sin^2 \omega t dt$$

$$= 0$$


AC through RL circuit

$$V = \sqrt{V_R^2 + V_A^2}$$

$$= \sqrt{(I R)^2 + (I \cdot x_L)^2}$$

$$= I \sqrt{R^2 + x_L^2}$$

$$I = \frac{V}{\sqrt{R^2 + x_L^2}}$$

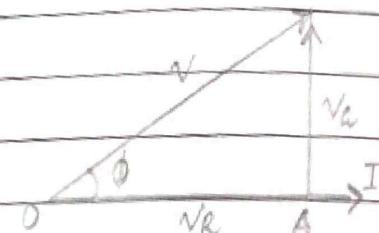


The quantity $\sqrt{R^2 + (x_L)^2}$

is known as the


impedance (Z) of the

circuit.

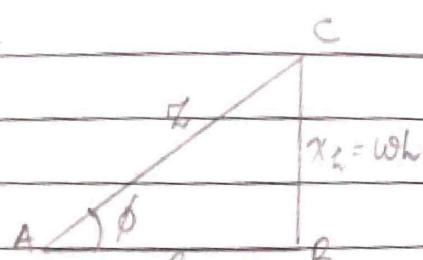

$$Z^2 = R^2 + x_L^2$$

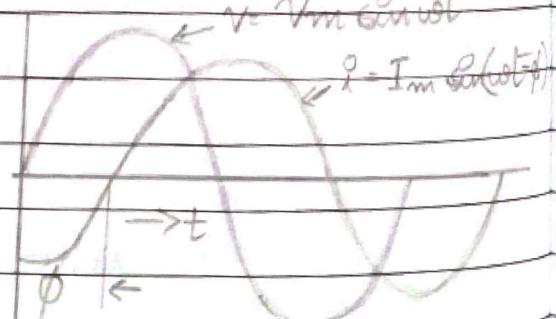the applied voltage V
leads current I by
an angle ϕ such that



$$\begin{aligned}\tan \phi &= \frac{V_R}{V_R} = \frac{I \cdot X_L}{I \cdot R} \\ &= \frac{X_L}{R} \\ &= \frac{\omega L}{R}\end{aligned}$$

Reactance
Resistance

$$\phi = \tan^{-1} \frac{X_L}{R}$$

I has been resolved into its two mutually perpendicular components, $I \cos \phi$ along the applied voltage V and $I \sin \phi$ in quadrature.

The mean power consumed by the circuit is given by the product of V and that component of the current I which is in phase with V.

$$\begin{aligned}P &= V \times I \cos \phi \\ &= \text{rms voltage} \times \text{rms current} \times \cos \phi\end{aligned}$$

Q-factor of a coil

$$\text{Q-factor} = \frac{1}{\text{power factor}}$$

$$= \frac{1}{\cos \phi} = \frac{Z}{R}$$

$$Q = 2\pi \times \frac{\text{maximum energy stored}}{\text{energy dissipated per cycle}}$$

Power Factor

Cosine of the angle of lead or lag

The ratio $\frac{R}{Z}$ = resistance
impedance

The ratio $\frac{\text{true power}}{\text{apparent power}} = \frac{\text{watts}}{\text{volts-ampere}} = \frac{W}{VA}$

Active and Reactive Components of Circuit current I

- Active component is that which is in phase with the applied voltage V i.e. $I \cos \phi$.
- It is also known as 'wattful' component.
- Reactive component is that which is quadrature with V i.e. $I \sin \phi$.
- It is also known as 'wattless' or 'idle' component.

Active, Reactive and apparent Power

- Apparent power (s)


It is given by the product of s.m.s values of applied voltage and circuit

current.

$$S = VI$$

$$= (IZ) \cdot I$$
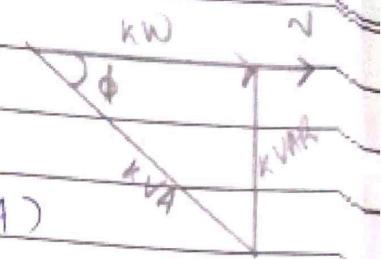
$$S = (IZ) \cdot I = I^2 Z \text{ volt-amperes (VA)}$$



active power (P or w)

Active component which is obtained by multiplying kVA by $\cos\phi$ and this gives power in kW.

$$P = I^2 R$$

$$= VI \cos\phi \text{ watts.}$$

Reactive power (Q)

The reactive component known as reactive kVA and is obtained by multiplying kVA by $\sin\phi$.

It is written as kVAR (kilo VAR)

$$Q = I^2 X_L$$

$$= I^2 \times Z \sin\phi$$

$$= I \times (IZ) \sin\phi$$


$$= VI \sin\phi \text{ volt-amperes-reactive (VAR)}$$

A.C through RC Series Circuit

$$V = \sqrt{V_R^2 + (-V_C)^2}$$

$$= \sqrt{(IR)^2 + (-IX_C)^2}$$

$$= I \sqrt{R^2 + X_C^2}$$

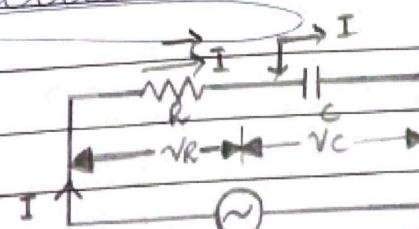


$$I = \frac{V}{\sqrt{R^2 + X_C^2}}$$

$$= \frac{V}{Z}$$

$$Z = \sqrt{R^2 + X_C^2}$$

Current leads voltage by ϕ

$$\tan \phi = -\frac{X_C}{R}$$

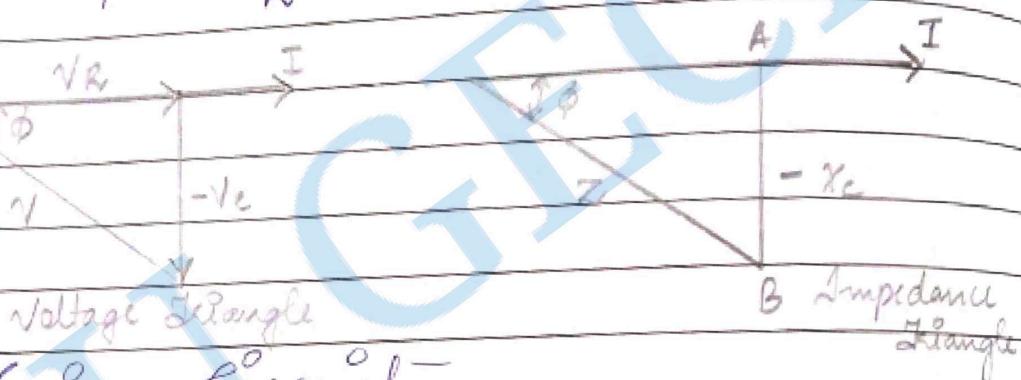


R.L.C Series Circuit

$V_R = IR$ = voltage drop across R - in phase with I

$V_L = I \cdot X_L$ = voltage drop across L - leading I by $\frac{\pi}{2}$

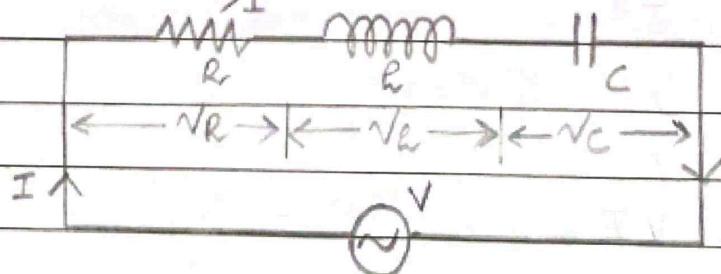$V_C = I \cdot X_C$ = voltage drop across C - lagging I by $\frac{\pi}{2}$.



$$OQ = \sqrt{OA^2 + AD^2}$$

OR

$$V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$= I \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{V}{\sqrt{R^2 + X^2}} = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

(Impedance)² = (Resistance)² - (net reactance)²

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$Z = \sqrt{R^2 + X^2}$$

phase angle ϕ

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$\frac{X}{R}$$

= net reactance
resistance

Power factor is $\cos \phi = \frac{R}{Z}$

$$= \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{R}{\sqrt{R^2 + X^2}}$$

resulting current in an R-L-C circuit is
given by $I = I_m \sin(\omega t \pm \phi)$

The +ve sign is to be used when current

leads i.e. $x_L > x_C$

- The -ve sign is to be used when current lags i.e. when $x_L > x_C$.

Symbolic notation : $Z = R + j(x_L - x_C)$

$$Z = \sqrt{R^2 + (x_L - x_C)^2}$$

If phase angle is $\phi = \tan^{-1} \left[\frac{x_L - x_C}{R} \right]$

$$Z = Z \left[\tan^{-1} \left[\frac{x_L - x_C}{R} \right] \right]$$

$$\cdot Z \left[\tan^{-1} \left(x_L/R \right) \right]$$

$$\text{if } V = V_{L0}$$

$$\text{then } I = \frac{V}{Z}$$

Summary of Results of Series AC Circuits


Type of impedance	Value of impedance	phase angle for current	Power factor
Resistance only	R	0°	1
Inductance only	jwL	90° lag	0
Capacitance only	1/jwC	90° lead	0
Resistance and Inductance	$\sqrt{R^2 + (wL)^2}$	$0 < \phi < 90^\circ$ lag	$1 > p.f > 0$
Resistance & Capacitance	$\sqrt{R^2 + (-1/wC)^2}$	$0 < \phi < 90^\circ$ lead	$1 > p.f > 0$
R, L, C	$\sqrt{R^2 + (wL - 1/wC)^2}$	btw 0° & 90° lag or lead	b/w 0 and unity lag or lead.

Three Phase System


comparison between polyphase system
and single phase system.

Poly phase system	single phase system
Power generation is cheaper	Power generation is costly.
High pf of efficiency	low pf of efficiency
Uses less material for a given capacity.	uses more material
Apparatus are economical.	Apparatus are costly.
Polyphase motors have uniform torque.	Pulsating torque
Parallel operation is very smooth.	Not smooth.

Production of Three Phase Voltage

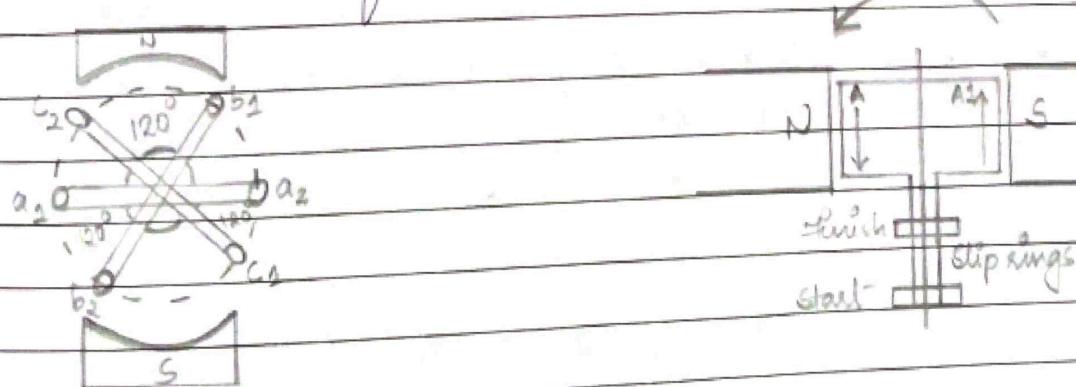

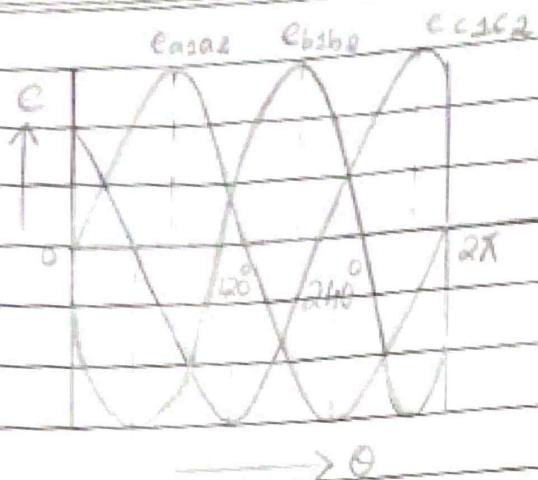- E_{a1} = E_m sin θ
- E_{b1} = E_m sin(θ - 120)
- E_{c1} = E_m sin(θ - 240)




$E_m(a_1a_2)$

$E_m(a_2a_2)$

$E_m(b_1b_2)$


Phase Sequence or phase order

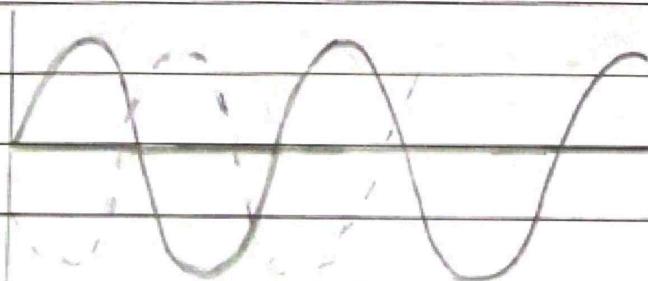- phase sequence is meant the order in which the three phases attain their peak or maximum positive values.
- The phase sequence can be reversed by interchanging any pair of lines.





Star Connected System

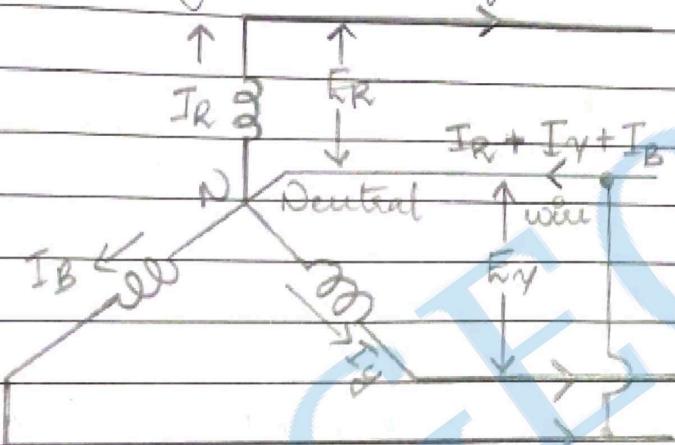The similar ends 'start' ends of three coils (it could be 'finishing' ends also) are joined together at point N.



Phase Voltage and line voltage

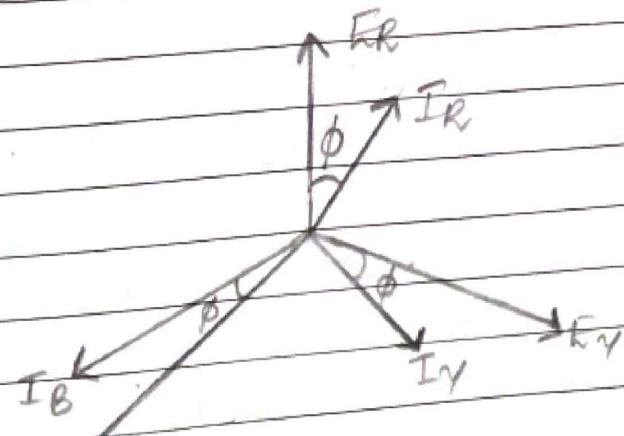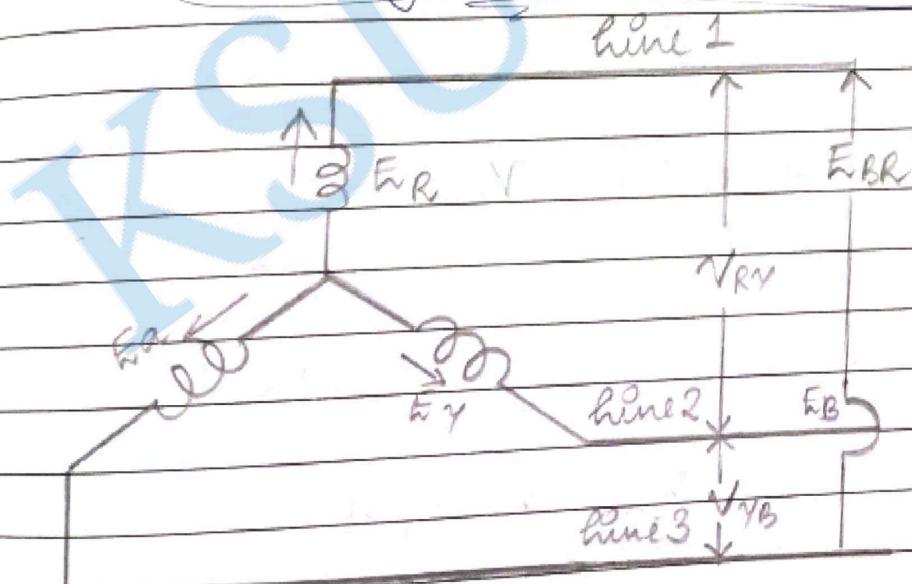


If $E_R = E_Y = E_B$
let E_{ph} be the phase e.m.f.,

$$V_{RY} = 2 \times E_{ph} \times \cos(60^\circ/2)$$

$$= 2 \times E_{ph} \times \cos 30^\circ$$

$$= 2 \times E_{ph} \times \frac{\sqrt{3}}{2}$$

$$= \sqrt{3} E_{ph}$$

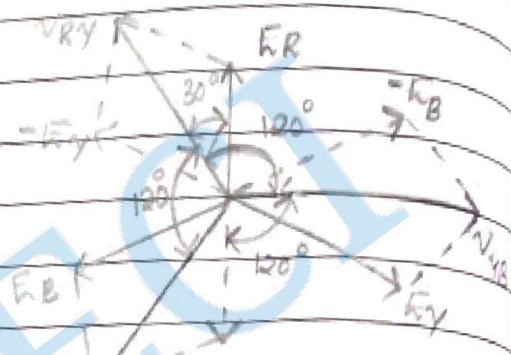

Similarly,

$$V_{YB} = E_Y - E_B$$

$$= \sqrt{3} \cdot E_{ph}$$
 [vector difference]

$$\text{if } V_{BR} = E_B - E_R \\ = \sqrt{3} \cdot E_{ph}$$

where V_{RY} , V_{YB} , V_{BR} are line voltages,
generally represented as V_a

Hence star connection,


$$V_L = \sqrt{3} E_{ph}$$

Note:

- Line voltages are 120° apart.
- Line voltages are 30° ahead of their respective phase voltages.
- The angle between the line currents and the corresponding line voltages is

$(30 + \phi)$ with current lagging.

line currents and phase currents

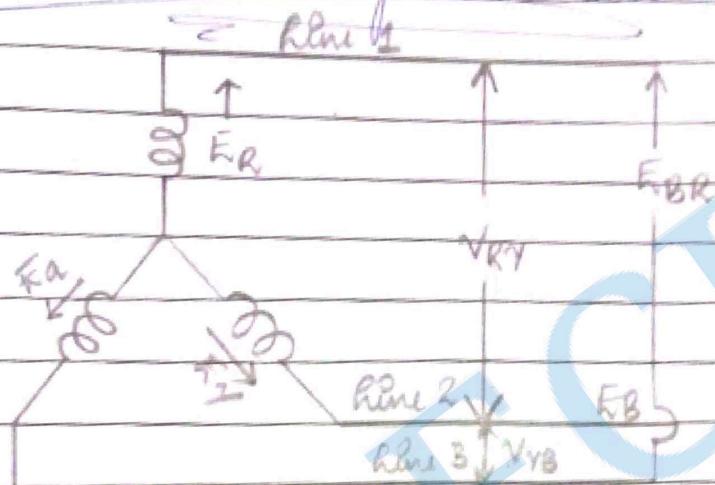

each line is in series with its individual phase winding, hence the line current in each line is the same as the current in the phase winding to which the line is connected.

Current in line 1 = I_R

Current in line 2 = I_Y

Current in line 3 = I_B

Since $I_R = I_Y = I_B$

Assume, I_{ph} be the phase current

\therefore line current $I_L = I_{ph}$

Power

The total active or true power in the circuit is the sum of the three phase powers. Hence, total active power = 3 × phase power,