



"The learning companion "

www.ktunotes.in

MODULE - 1

(9) new (18)

Basic concepts regarding electrical

- 1) charge - Electrical property of a substance
 2) current
 3) Voltage
 4) power
 5) Energy

1) charge (q)

Electrical property of a substance.

unit coulomb (C)

$$[Q = IT]$$

2) Current (I)

It is the directed flow of free e⁻s. Its direction is just opposite to the flow of e⁻.

$$[I = q/t]$$

3) Voltage / emf / potential (V)

workdone per charge (work/charge)

unit = C/C or Volt.

$$[V = \frac{W}{q}]$$

A (+5) ————— B (-3)

Pd b/w A & B

$$V_{AB} = V_A - V_B \\ = 5 - 3 = 2V$$

4) power (P)

E = J/VOM

Rate of doing work is called as power

$$P = VI$$

unit = J/sec or watts

5)

Energy (E)

Capacity to do work

$$E = P \cdot t$$

unit = J / wh (watt-hour) / kwh

1 unit = 1 kwh.

Circuit

It is a closed path. It is the interconnection of various circuit elements.

Circuit elements can be of 2 types

- 1) passive elements :- element that doesn't generate energy. Eg: Resistor, inductor & capacitor.
- 2) Active elements

↓
(V) battery & generator
capable of generating energy

Eg: Battery, Generator etc.

RESISTOR

Resistance (R) :- ~~resistance, diff - in~~

It is a property of a substance A by which it opposes the flow of current

unit = ohm (Ω)

one Ω

Resistance of a material depends upon

(Q) ~~to~~ ~~order~~ ~~size~~

1) length , $R \propto L$

2) Area , $R \propto 1/A$

3) Nature of the material

4) Temp.

Resistivity $R \propto L/A$

$$R = \rho \frac{L}{A}$$

ρ = Resistivity / specific Resistance of the material

$$\rho = \frac{RA}{L} = \Omega m^2/m$$

$$\boxed{\rho = \Omega m^2/m}$$

Conductance (G_1) :-

REVISION

It is the reciprocal of Resistance.

$$G_1 = \frac{1}{R}$$

Ohm's Law

(V and I are in SI units)

It states that the ratio of p.d (V) applied across the ends of the conductor to the current flowing through the conductor (I) is always a constant.

OR

Ohm's law states that the p.d applied across the ends of the conductor is directly proportional to the current flowing through it.


$$\frac{V}{I} = \text{a const} \Rightarrow \boxed{\frac{V}{I} = R}$$

$V \propto I$

$$\boxed{V = IR}$$

$$\begin{aligned} P &= VI \\ P &= I^2 R \\ P &= \frac{V^2}{R} \end{aligned}$$
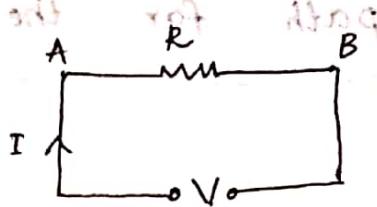
$$\begin{aligned} P &= IR \cdot I \\ P &= I^2 R \\ P &= \frac{V^2}{R} \end{aligned}$$



DC CIRCUIT


A circuit consists of the following components

- 1) Source of power
- 2) conductor for carrying current
- 3) load.

There are 2 types of DC circuit

- 1) DC series circuit
- 2) DC parallel circuit

DC Series Circuit

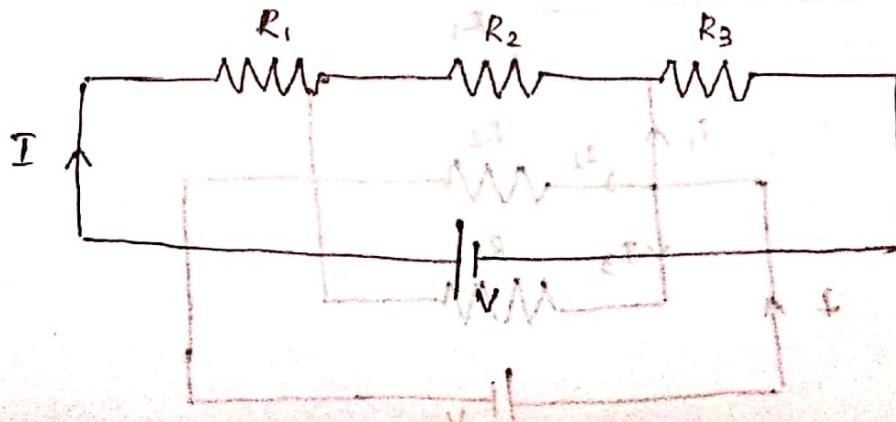

In a Series circuit each resistance are connected end to end such that there is only one path for the current through the circuit.



Let V_1 , V_2 , & V_3 be the voltages across R_1 , R_2 & R_3 respectively. Then

$$V = V_1 + V_2 + V_3$$


$$IR = IR_1 + IR_2 + IR_3$$

$$R_s = R_1 + R_2 + R_3$$

where R_s is the total or equivalent resistance of the Series Circuit.


$$\text{Power (P)} = P_1 + P_2 + P_3$$

Dc parallel circuit

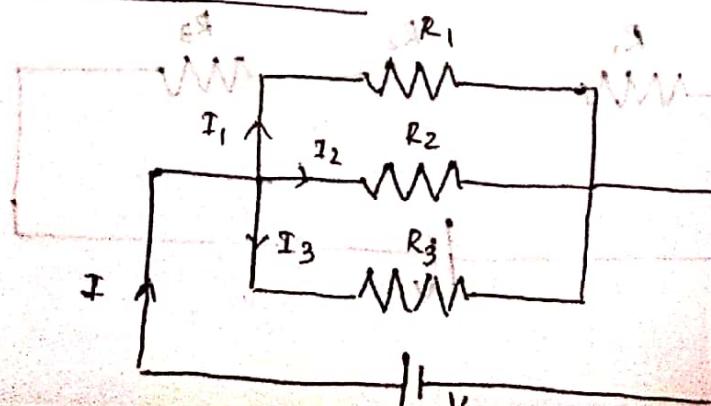

In parallel circuit one end of each resistor is connected to a common point & other end to another common point ~~up so~~, that current in the circuit will have different paths.

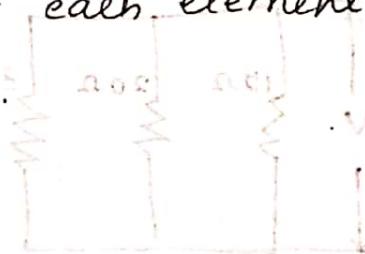Voltage across each element is same in a parallel circuit.



$$\text{Total current } (I) = I_1 + I_2 + I_3$$


$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

i.e; Reciprocal of Total resistance in a parallel circuit equal to the sum of the reciprocals of individual resistances.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

*
$$R = \frac{R_1 R_2}{R_1 + R_2}$$

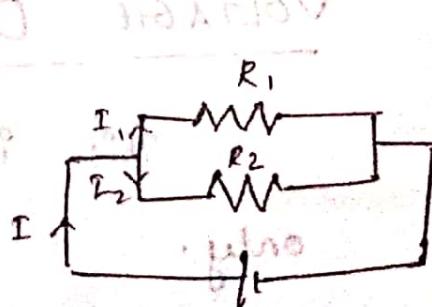


$$P = P_1 + P_2 + P_3$$

↳ Represents a circuit formed by jointing resistors.

* Find the equivalent resistance of the given parallel network and also draw the circuit.

∴ ans is

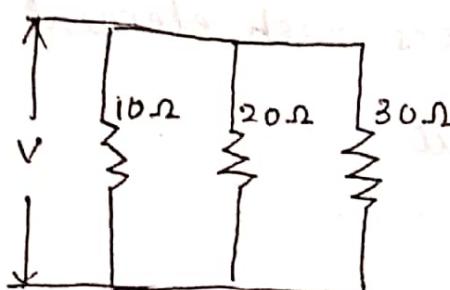

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_{\text{eq}}} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30}$$

$$= 0.1 + 0.05 + 0.0333$$

$$\text{Then } \frac{1}{R_{\text{eq}}} = \underline{\underline{0.1833}} \quad 0.1833$$

$$\therefore R_{\text{eq}} = \underline{\underline{5.4545}} \Omega$$

VOLTAGE DIVISION RULE

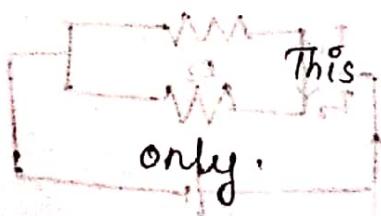


This is applicable in series circuits

only.



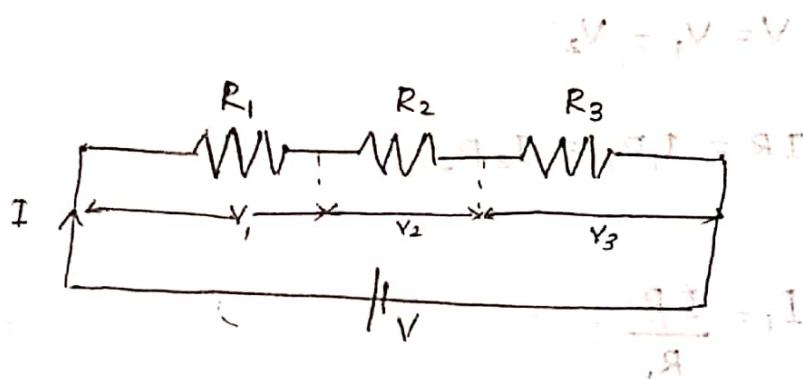If we have 2 resistances R_1 & R_2 connected in series and V be the total voltage applied across the combinat'. Let I be the current flowing through the circuit. According to Voltage divider rule



$$V_1 = IR_1$$


$$V_1 = \frac{V}{R} R_1$$

$$V_1 = \left(\frac{V}{R_1 + R_2} \right) R_1 = \frac{\text{Total Voltage}}{\text{Total Resist}} \times R_1$$

$$V_2 = \left(\frac{V}{R_1 + R_2} \right) R_2$$

CURRENT DIVISION RULE

It is applicable only in DC circuit.

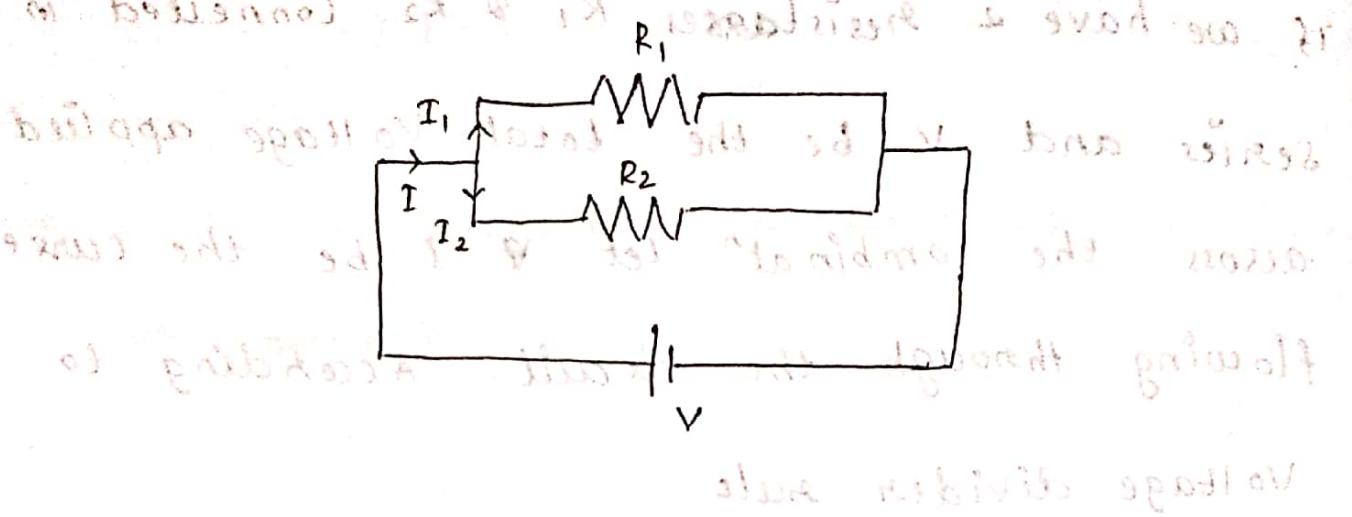

$$V = V_1 = V_2$$

$$IR = I_1 R_1 \neq I_2 R_2$$

$$I_1 = \frac{IR}{R_1}$$


where R is the equivalent resistance of the parallel combination.

$$I_1 = I \left[\frac{R_1 R_2}{R_1 + R_2} \right] = \frac{I R_1 R_2}{R_1 (R_1 + R_2)}$$

$$I_1 = \frac{IR_2}{R_1 + R_2}$$

$$I_2 = \frac{IR_1}{R_1 + R_2}$$

*

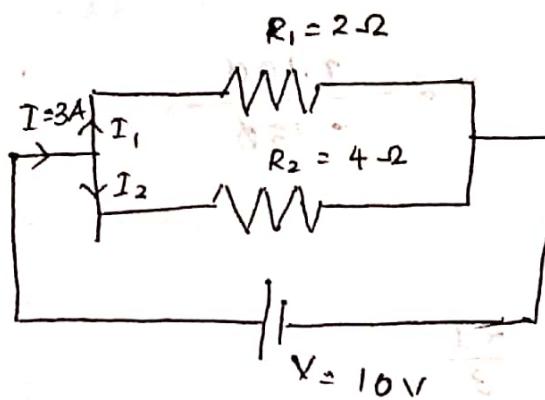

$$I_1 = ?$$


$$I_2 = ?$$

$$\rightarrow I_1 = \frac{I R_2}{R_1 + R_2} = \frac{3 \times 4}{6} = \frac{12}{6} = 2 \text{ A}$$

$$I_2 = \frac{I R_1}{R_1 + R_2} = \frac{3 \times 2}{6} = \frac{6}{6} = 1 \text{ A}$$

- * A 50Ω resistor is in llc with a 100Ω resistor. Current in 50Ω is 7.2 A . What is the value of third resistance to be added in llc to this circuit to make total current 12.1 A

\rightarrow

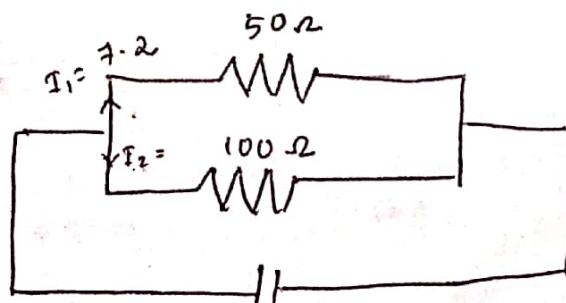

$$\frac{8000}{150} = 33.3$$

$$12.1 - 70.7 = 1.3$$

$$I_1 = \frac{IR_2}{R_1+R_2} = I \cdot 2 = \frac{I \times 10\Omega}{15\Omega}$$

$$I \cdot 2 = \frac{10I}{15\Omega} = \frac{2I}{3} \text{ A}$$

$$\frac{2I \cdot 6}{2} = I = \underline{\underline{10.8}} \text{ A}$$

$I = 10.8$

$E = 12V$

$$I_2 = \frac{IR_1}{R_1+R_2} = \frac{10.8 \times 5\Omega}{15\Omega} = \frac{10.8}{3} = \underline{\underline{3.6}} \text{ A}$$

$$I_3 = \frac{IR_{12}}{R_{12}+R_3} = \frac{12V \times 15\Omega}{33.3 + R_3} \quad \text{if } R = \frac{R_1R_2}{R_1+R_2}$$

$$= 33.3$$

$$8.5 = \frac{18.5}{15\Omega + R_3} \quad 402.93$$

Now we have to find the value of R_3 in ohms

$$15\Omega + R_3 = \frac{18.5}{8.5} = 213.5$$

But we have to find the resistance in ohms

$$47.40 - 33.3$$



$$V = IR$$

GRADUATE

$$V = V_1 = V_2 = V_3$$

Since all resistances are in series, we can add them up to get total resistance.

$$V_1 = I_1 R_1$$

$$V = IR$$

$$\text{substituting } IR = V/I \text{ in}$$

(series)

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

After adding up all resistances, we get total resistance.

$$IR = \frac{2R_1}{R_1 + R_2}$$

$$= \frac{(2 \cdot 1 \times 50)}{50 + 100} = 4.034 \text{ A}$$

$$I_1 = I_1 + I_2 + I_3$$

Given current through I_2 is 7.2 A

$$12.1 = 7.2 + 4.03 + I_3$$

$$= 0.87$$

$$I_1 = \frac{IR}{R_1} = 7.2 = \frac{12.1 R}{50}$$

After calculating total resistance, we get

$$R = 29.75$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Given resistances are 50, 100 and 29.75 ohms

$$\frac{1}{R_3} = \frac{1}{50} - \frac{1}{100} - \frac{1}{29.75} = \frac{3.61}{1000} = 277 \Omega$$


So, the value of R_3 is 277 ohms.

INDUCTOR

$\Delta V = V$

is

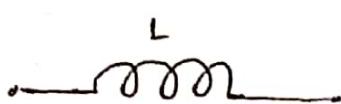A conductor twisted to form a basic inductor. This is usually denoted by the letter L



(mag field produced around)

when a current 'I' flows through the inductor a mag field \mathbf{B} will be set up around that inductor

$$\therefore \boxed{\text{Inductance } 'L' = \frac{N\phi}{I}} \Rightarrow \text{Henry (unit)}$$

N = no. of turns of the coil

I = Current

ϕ = mag flux in webbes

when current I through the inductor increases mag field expands & when the current decreases mag field will reduce.

i.e; whenever there is a change in current, there will be a change in mag flux. According to Faraday's laws of

electromagnetic Induction,

An emf (Voltage) is induced in the inductor. ie; Voltage across the inductor be proportional to $\frac{di}{dt}$

$$V \propto \frac{di}{dt}$$

$$V = L \frac{di}{dt}$$

COTIDARAO

(1)

power absorbed in the inductor


$$P = VI$$

$$= L \frac{di}{dt} i$$

Voltage between terminals of inductor

$$P = L i \frac{di}{dt}$$

(2) part of second

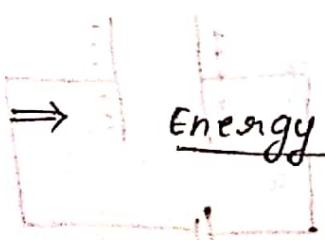

Energy abs (E)

$$E = Pt$$

$$E = \int_0^t P dt$$

$$P = \frac{E}{t}$$

$$E = \int_0^t L_i^0 \frac{di}{dt} dt$$

calculated by integration

at any instant (instant) it finds the value of current at that instant and $E = \frac{1}{2} L_i^0 i^2$ is calculated.

$$E = \frac{1}{2} L_i^0 i^2$$


CAPACITOR

Two conducting plates are separated by a dielectric medium \Rightarrow capacitor.

It is used to store electric charge.

Let Q be the charge stored on the capacitor & V be the potential applied across the capacitor.
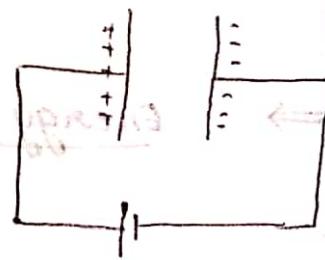
$$C = \frac{\text{charge}}{\text{voltage}} = \frac{Q}{V}$$



$$C = \frac{Q}{V} \rightarrow \text{Faraday's Law}$$

\Rightarrow Current through the capacitor

definition $I = \frac{dQ}{dt}$

$$I = C \frac{dV}{dt}$$

and $C = \frac{Q}{V}$ \therefore current $I = \frac{dQ}{dt} = \frac{d(CV)}{dt}$

or $Q = CV$ \therefore current $I = \frac{d(CV)}{dt}$

\Rightarrow so $I = C \frac{dV}{dt}$ \therefore current \propto voltage

\Rightarrow power \propto current \times voltage

$P = VI$

$$= C \frac{dV}{dt} V C \frac{dV}{dt}$$

$$P = C V \frac{dV}{dt}$$



\Rightarrow Energy

$$E = Pt$$

$$E = \int_0^t Pt dt = \int_0^t C V \frac{dV}{dt} dt$$

standard form $E = \frac{1}{2} CV^2$

$$E = \frac{1}{2} CV^2$$


$$E = \frac{1}{2} CV^2$$

CONSTANT VOLTAGE SOURCE (Ideal Voltage source)

It is defined as the energy source whose terminal voltage is independent of the current through it. It means that when the current drawn from the source varies from zero to infinity, the terminal voltage of the source remains unaffected. An Ideal Voltage source has zero internal resistance.



const. dc
Voltage source

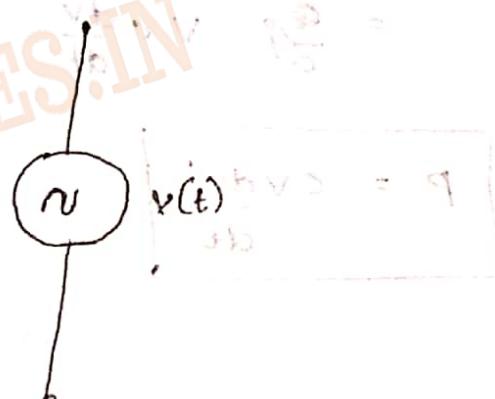


const. Ac
Voltage source


PRACTICAL VOLTAGE SOURCE (Real Voltage source)

It has low but finite internal resistance that causes its terminal voltage to rise when the load current is passed.

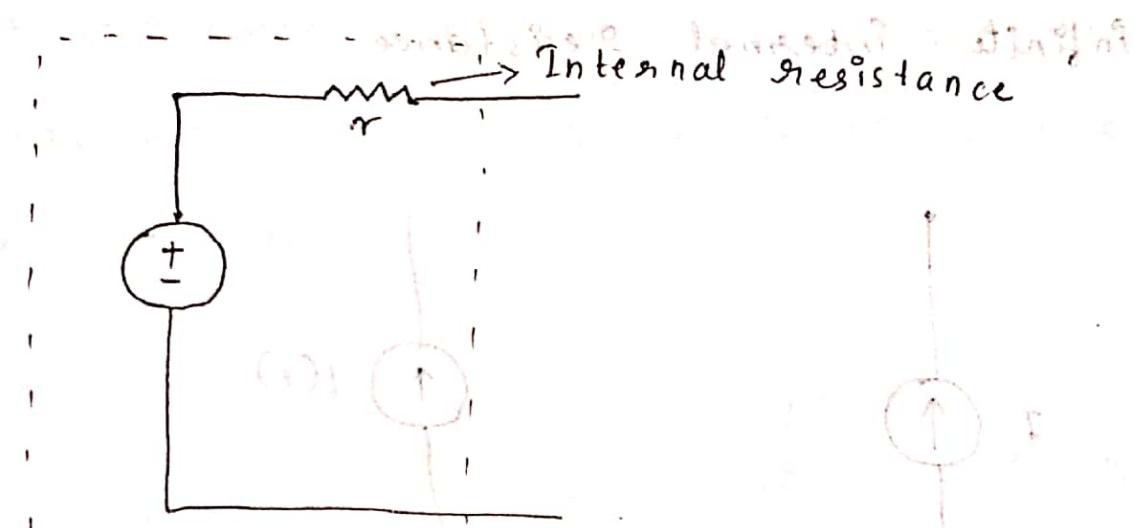Vice Versa. It can be represented by an ideal Voltage Source in series with a resistance.




DC voltage source.

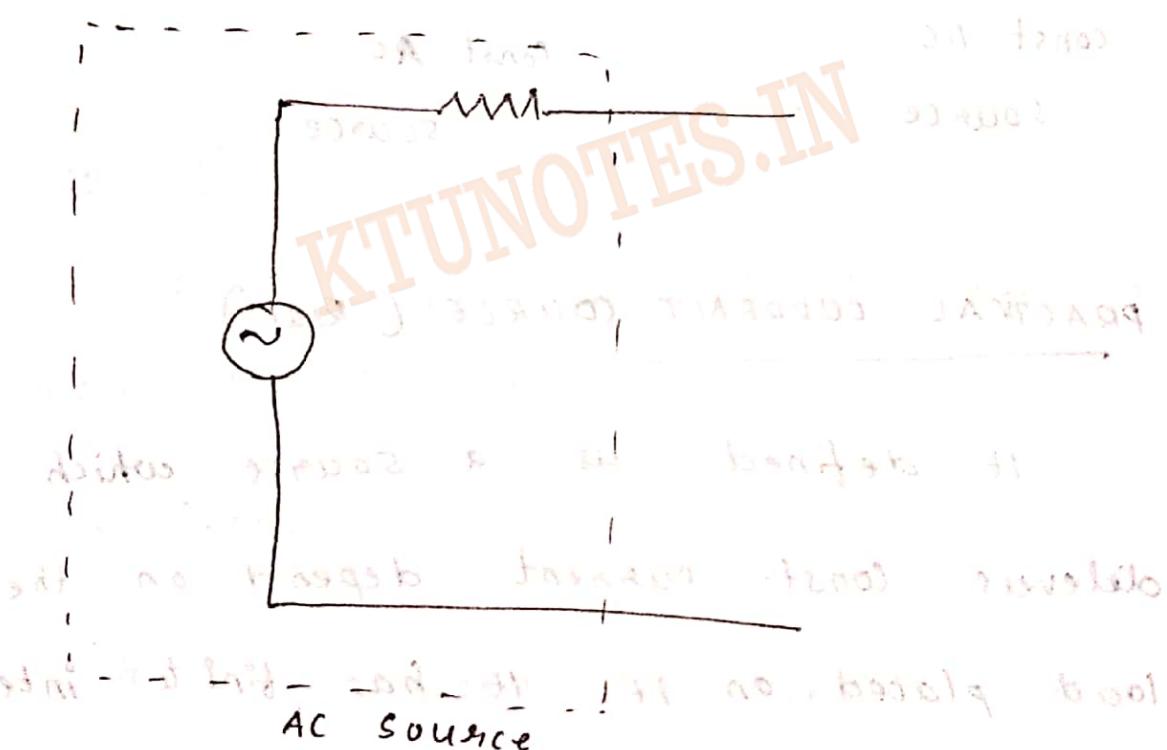

CONSTANT (IDEAL) CURRENT SOURCE

It is defined as a source which delivers constant current independent of the load placed on it. Thus the output

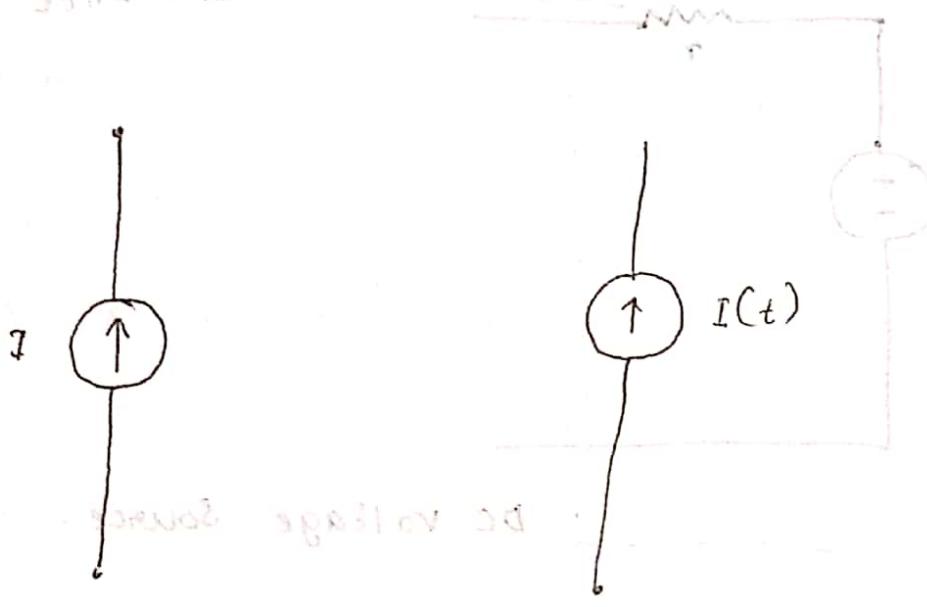current of such a source remains unaltered from zero to infinity of load. It has infinite internal resistance.



const. DC

source

$$I(t)$$


const. AC

source

PRACTICAL CURRENT SOURCE (Real)


It defined as a source which delivers const. current depend on the load placed on it. It has finite internal resistance.

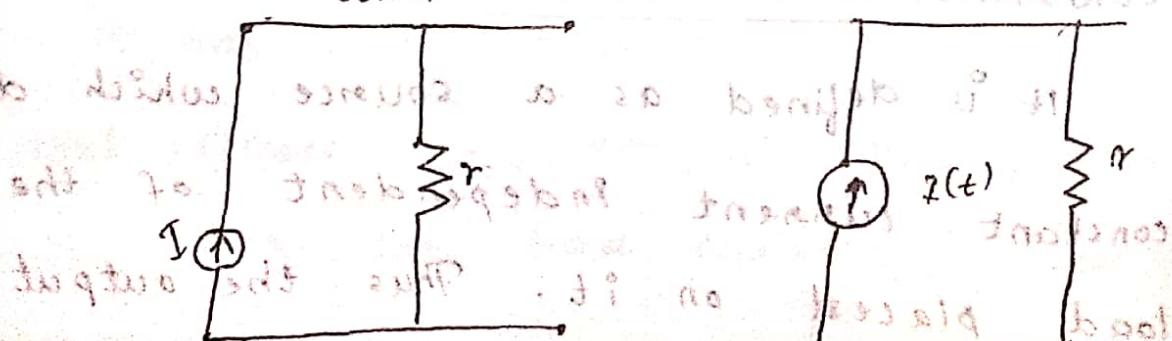const. DC source (Ideal) to const. ac source.



SOURCE CONVERSION

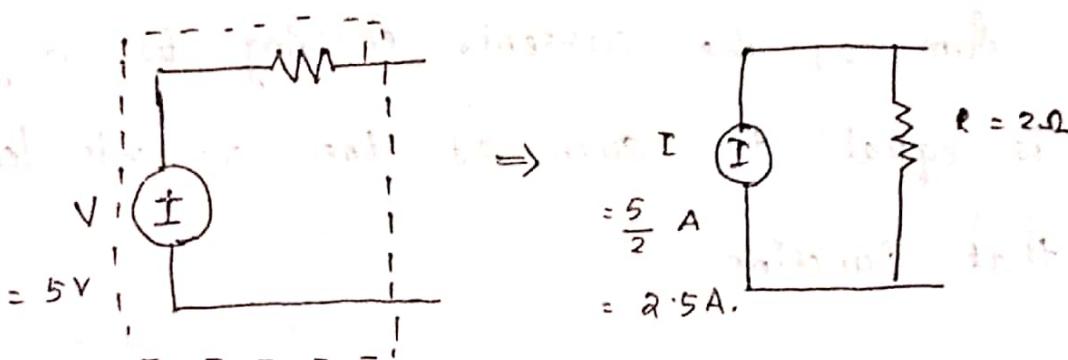If we have a voltage source in series with a resistance can be converted into an equivalent current source in parallel with a resistor and vice versa.



NODE (Junction)

It is a point in a circuit where two or more elements meet

LOOP (Mesh)

It is a closed path in a circuit

KIRCHHOFF'S LAW

There are 2 laws

First law : Kirchoff's Current Law (KCL) or Junction Rule.

It is associated with current in a circuit.


The law states that the algebraic sum of the currents meeting at a point (node) is always zero.

OR

Sum of the currents entering to a junction is equal to sum of the currents leaving that junction.

The incoming currents can be taken as +ve & outgoing currents can be taken as -ve.

$$\sum I = 0$$

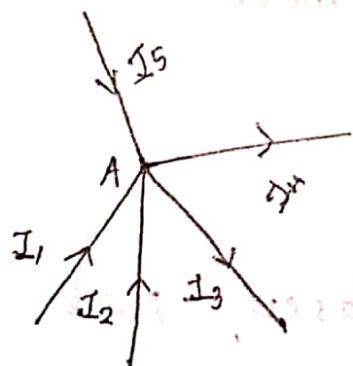

$$I_1 + I_2 - I_3 - I_4 + I_5 = 0$$

$$I_1 + I_2 + I_5 = I_3 + I_4$$

IInd Law : Kirchoff's Voltage Law (KVL)

It is associated with Voltages in a loop.

A diagram of a closed loop circuit. Inside the loop, there are two resistors represented by rectangles with arrows indicating current flow, and two voltage sources represented by circles with arrows indicating direction. The equation $\sum IR + \sum Emf = 0$ is written below the loop, with 'Voltage drop' and 'Source' labels pointing to the respective resistors and emfs.

$$\sum IR + \sum Emf = 0$$


KVL states that algebraic sum of Voltage drop across the resistors plus algebraic sum of emf in a closed mesh (loop) is always zero.

Sign Convention

①




$+IR \Rightarrow$ Rise in potential.

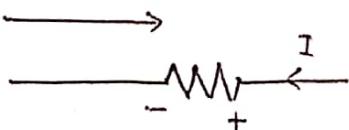

②

$-IR \Rightarrow$ Fall in potential.

③.

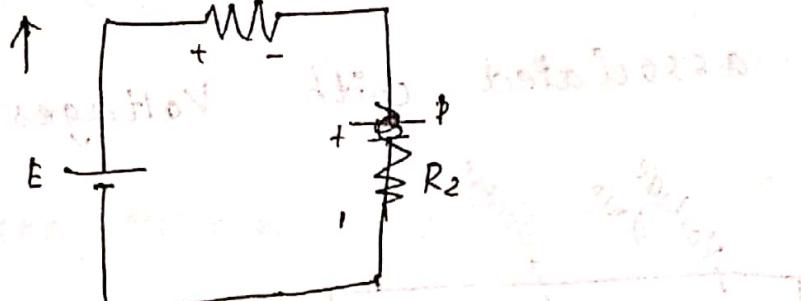


$$V_3 = IR_2 + E_V$$

$$+IR_1 + IR_2 - E_V = 0$$

$$IR_1 + IR_2 - E_V = 0$$

In (a) diagram $IR_1 + IR_2 = E_V$ or $I = \frac{E_V}{R_1 + R_2}$

④.

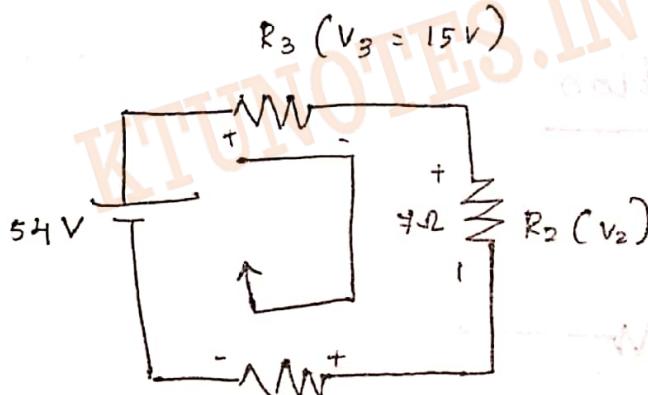

$$R_1 (V_1 = 18V)$$

Determine,

① V_2 using KVL

② current flowing in loop C

③ R_1 & R_3

$$IR_3 + IR_2 + IR_1 - E = 0$$

$$IR_3 + IR_2 + IR_1 = E$$

$$I(R_1 + R_2 + R_3) = 54V$$

∴

$$18 + V_2 + 15 = 54V$$

$$\begin{array}{r} 15 \\ 18 \\ \hline 33 \end{array}$$

$$V_2 = 54 - 15 - 18 \\ = \underline{\underline{21V}}$$

$$\begin{array}{r} 54 \\ 33 \\ \hline 21 \end{array}$$

$$IR_2 = 21V$$

$$R_2 = \frac{21}{I} = 7\Omega$$

$$I = 3A$$


$$IR_1 = 3 \times R_1$$

$$IR_1 = 18$$

$$R_1 = \frac{18}{3} = \underline{\underline{6\Omega}}$$

$$IR_3 = 15$$

$$R_3 = \frac{15}{3} = \underline{\underline{5\Omega}}$$

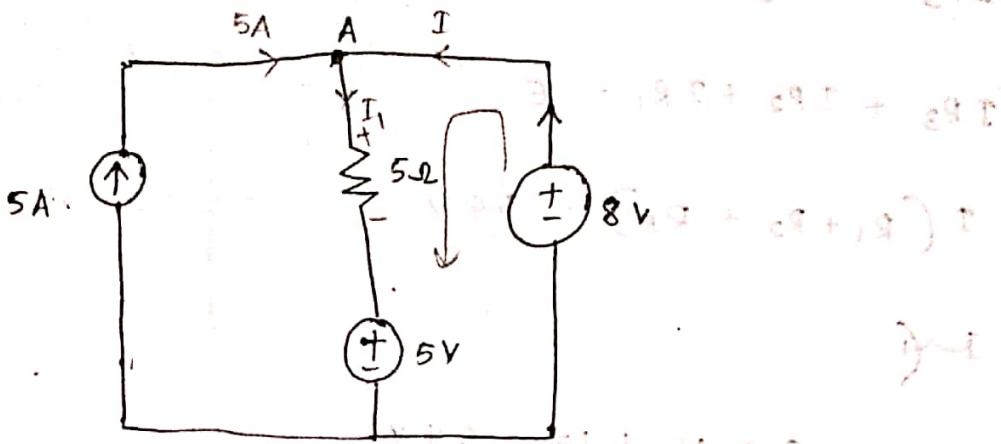

Find I

\rightarrow KCL at node A
and

$$+5A + I - I_1 = 0$$

$$5 + I = I_1 \quad \text{--- (1)}$$

KVL to 2nd mesh

$$5I_1 + 5 - 8 = 0$$

$$5I_1 = 3$$

$$I_1 = \frac{3}{5} \quad \text{--- (2)}$$

(2) in (1)




$$5 + I = \frac{3}{5}$$

$$\cancel{5} \frac{3}{5} = \frac{3}{5} - 5 = I$$


$$\frac{3 - 25}{5} = I$$

$$= -\frac{22}{5} = \underline{-4.4A} \quad \text{given direct' is opposite to the actual direction.}$$

Star to Delta & Delta to Star conversion

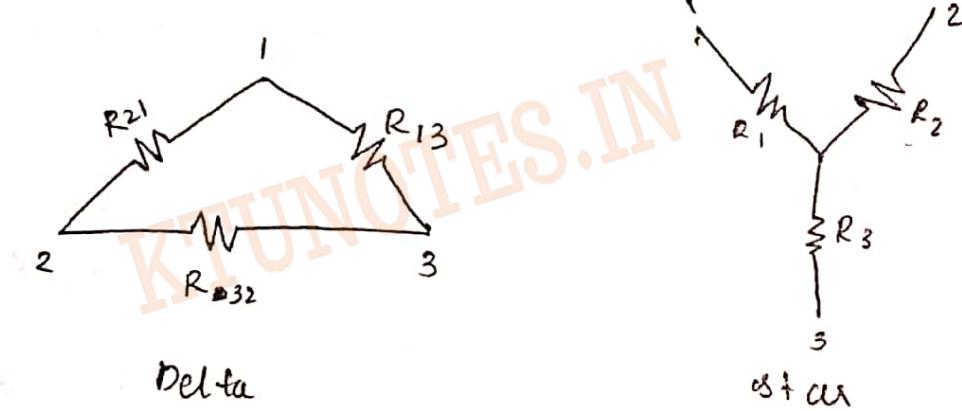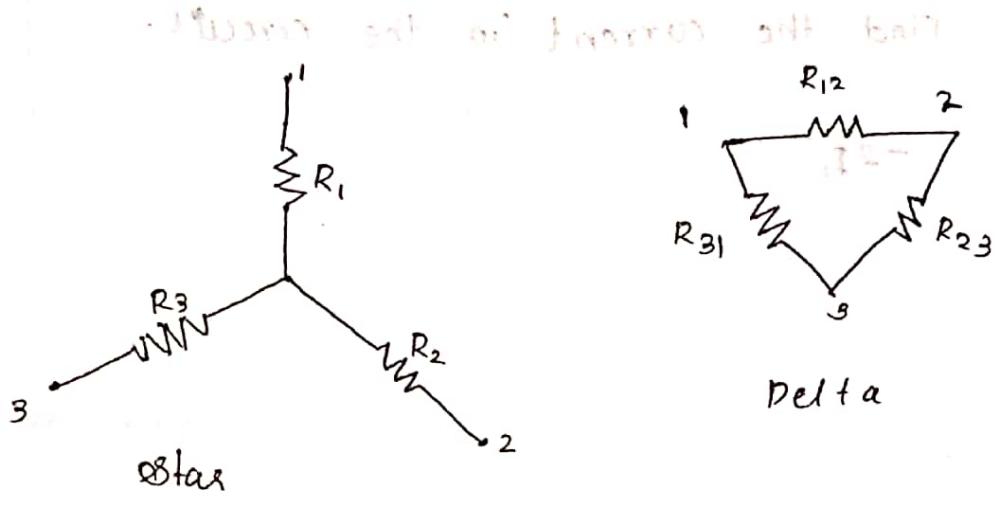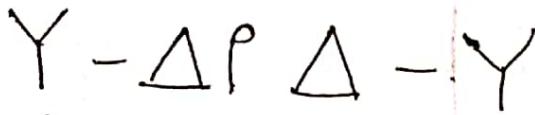

Star to Delta conversion

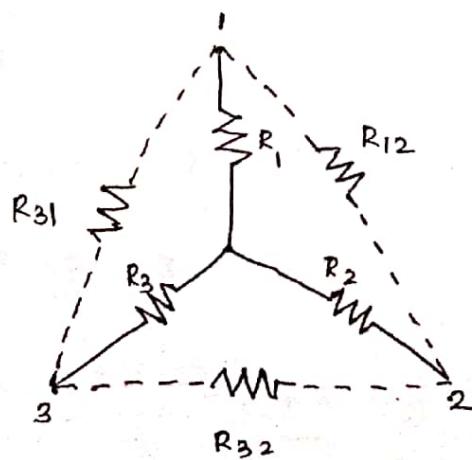


$$R_{12} = R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3}$$

$$R_{32} = R_3 + R_2 + \frac{R_3 \cdot R_2}{R_1}$$

$$R_{31} = R_3 + R_1 + \frac{R_3 \cdot R_1}{R_2}$$

Delta to Star conversion

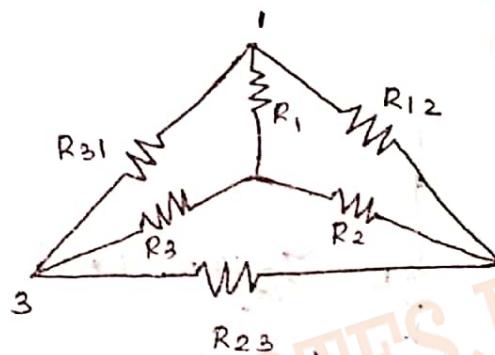


$$R_1 = \frac{R_{12} \cdot R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$R_2 = \frac{R_{23} + R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_3 = \frac{R_{23} + R_{31}}{R_{12} + R_{23} + R_{31}}$$

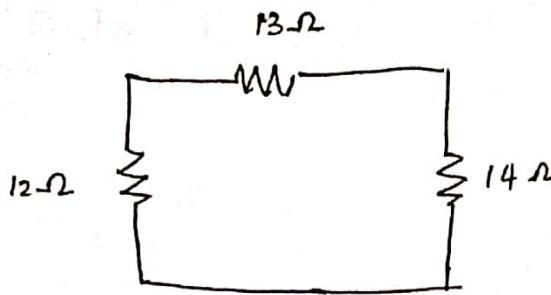- * obtain the total equivalent of a connected network as given.



→




(R₂₃)

(R₂₁)

2

13 ohm

(R₂₃)

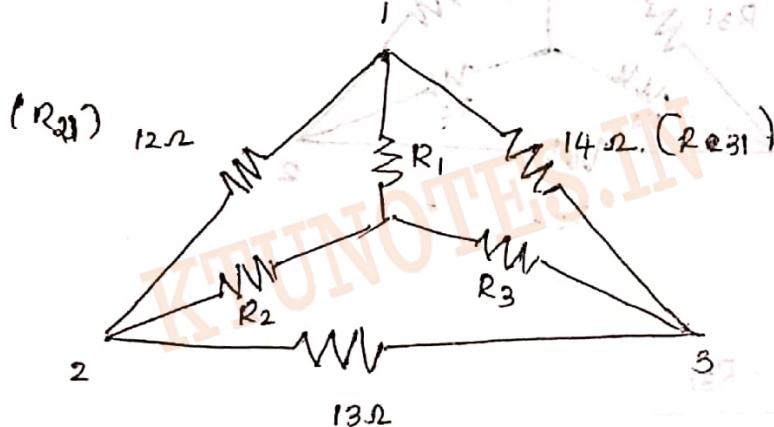


$$R_1 = \frac{R_{21} * R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{12 * 14}{12 + 14 + 13} = \frac{168}{39} = 4.3$$


$$R_2 = \frac{R_{21} + R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{12 + 13}{12 + 14 + 13} = \frac{156}{39} = 4$$

$$R_3 = \frac{R_{31} + R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{14 + 13}{12 + 14 + 13} = \frac{182}{39} = 4.6$$

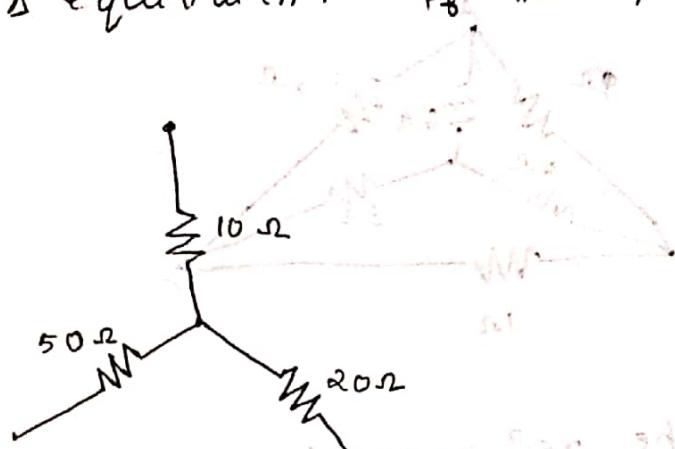* obtain the Δ equivalent of the γ network



\rightarrow

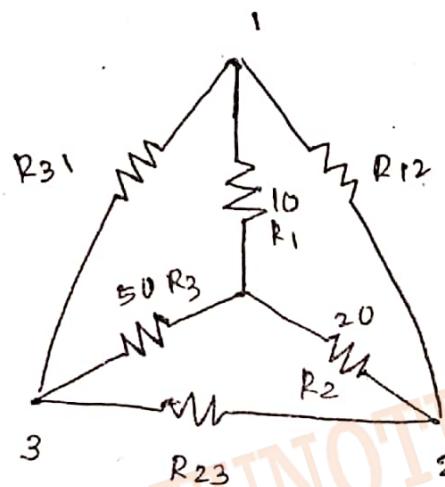


$$R_{31} = R_3 + R_1 + \frac{R_3 R_1}{R_2} = \underline{\underline{50 + 10 + \frac{50 \times 10}{20}}} \\ = \underline{\underline{85 \Omega}}$$

$$R_{12} = 10 + 20 + \frac{10 \times 20}{50} = \underline{\underline{34 \Omega}}$$

$$R_{23} = 20 + 50 + \frac{20 \times 50}{10} = \underline{\underline{170 \Omega}}$$

(Q)

→

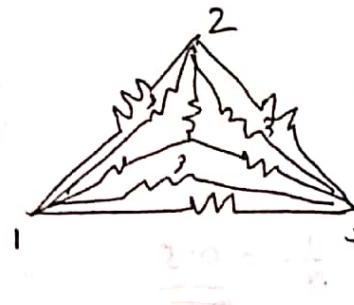


$$\frac{1}{R} + \frac{1}{3} = \frac{1}{2}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3}$$

$$= 1 + 1 + \frac{1}{1}$$

$$= \underline{\underline{3}}.$$

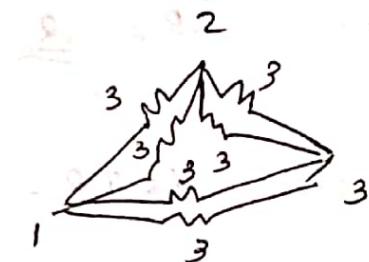

$$R_{32} = 3$$

$$R_{13} = 3$$

$$\frac{1}{R_{12}} = \frac{3}{3} + \frac{3}{3} = \frac{6}{9}$$

$$= \cancel{\frac{2+1}{2}} = \cancel{\frac{3}{2}} = \underline{\underline{1.5}}$$


R₁₂

$$R_{12} = \underline{\underline{0.67}}$$

$$R_{12} = \frac{9}{6} = \frac{3}{2} = \underline{\underline{1.5}}$$

$$R_{AB} = \frac{1.5 \times 3}{1.5 + 3} = \underline{\underline{1}}$$

Q)

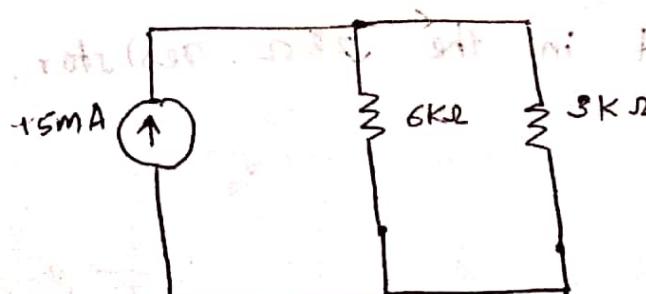

Find current in 6kΩ resistor.

$$\frac{1}{R} = \frac{1}{6} + \frac{1}{3}$$

$$\Rightarrow \frac{3+6}{18} = \frac{9}{18} = \frac{1}{\alpha} = 0.5$$


$$SR = \underline{\underline{2}}$$

$$V = IR = 15 \times 10^{-3} \times 2 \\ = \underline{\underline{30 \times 10^{-3}}}$$


$$I = \frac{V}{R_1} = \frac{30 \times 10^{-3}}{6}$$

$$= \underline{\underline{5mA}}$$

(q)

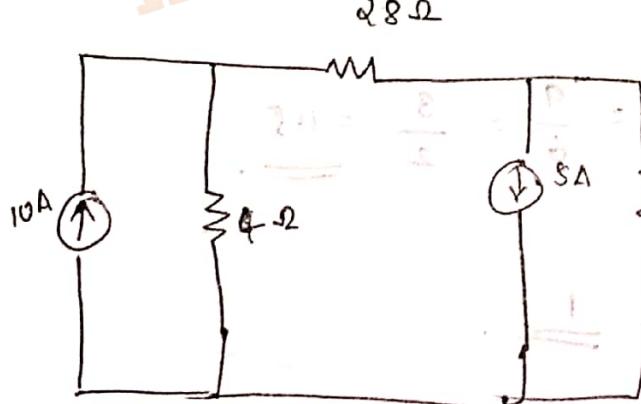


Find the current in the 28Ω resistor.

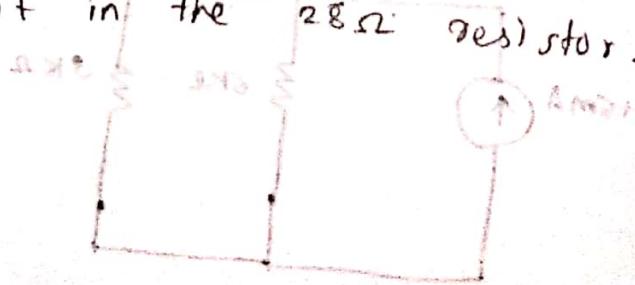

$$V_1 = \frac{I}{R} = \frac{105}{4\Omega} = \underline{\underline{\frac{5}{2}}} \text{ (Ans) at 30A load}$$

$$V_1 = I_1 R_1 = 10 \times 4 = \underline{\underline{40V}}$$

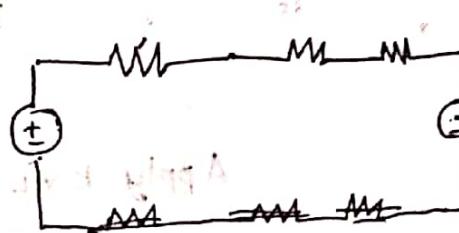
$$V_2 = I_2 R_2 = 5 \times 8 = \underline{\underline{40V}}$$



MESH CURRENT METHOD (Maxwell's loop current method)

This method is based on KVL. Ques: In this method 1st of all we have to identify the meshes. Then current in each mesh is assigned in the clockwise direction.

Eg:

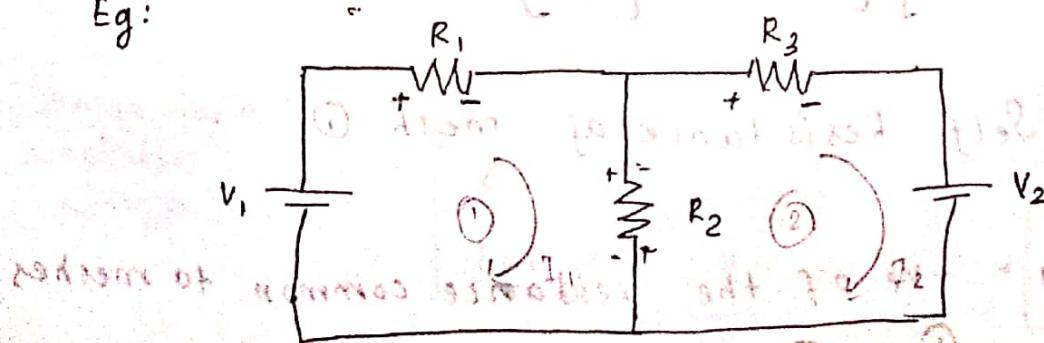

Apply KVL in mesh ①

$$I_1 R_1 + I_2 R_2 - I_2 R_2 - V_1 = 0 \quad \text{or} \quad I_1 R_1 = V_1$$

$$I_1 (R_1 + R_2) - I_2 R_2 = V_1 \quad \text{--- (1)}$$

Apply KVL in mesh ②

$$I_2 R_2 + I_2 R_3 - I_1 R_2 + V_2 = 0$$

$$- I_1 R_2 + I_2 (R_2 + R_3) + V_2 = 0$$

$$- I_1 R_2 + I_2 (R_2 + R_3) = -V_2 \quad \text{--- (2)}$$

Resultant Mesh Matrix Form

$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} +V_1 \\ -V_2 \end{bmatrix}$$

In general $[R][I] = [V]$

beginning is done along the first row column

$$\begin{bmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

R_{11} = Self Resistance of mesh ① (sum of all resistance in mesh ①)


$R_{12} = R_{21}$ = -ve of the resistance common to meshes ① & ②

(cal 01)
 R_{22} = self-resistance of mesh ②

$$I_1 = \frac{\Delta_1}{\Delta}, \quad I_2 = \frac{\Delta_2}{\Delta}$$

$$\Delta = \begin{vmatrix} R_{11} & R_{12} \\ R_{21} & R_{22} \end{vmatrix}, \quad \Delta_1 = \begin{vmatrix} V_1 & R_{12} \\ V_2 & R_{22} \end{vmatrix}$$
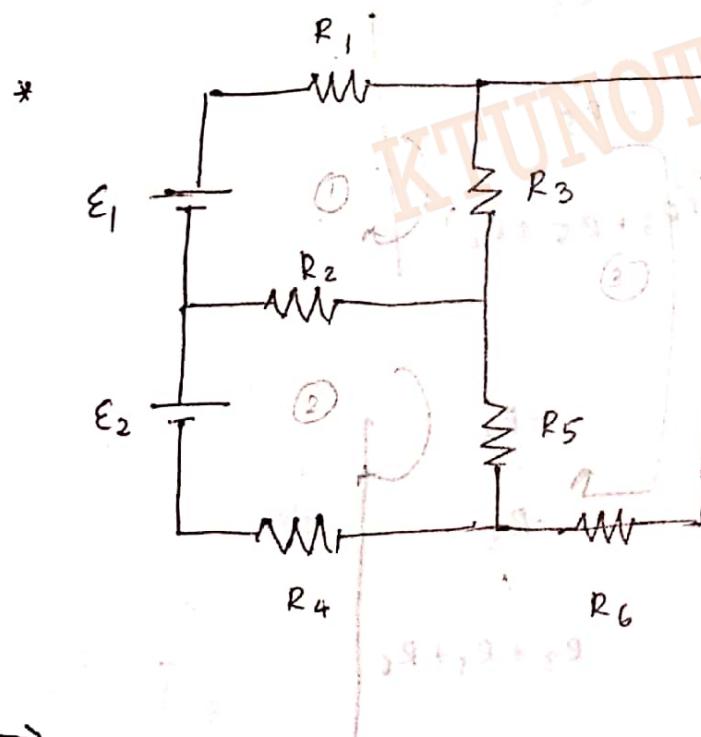
$$\Delta_2 = \begin{vmatrix} R_{11} & V_1 \\ R_{21} & V_2 \end{vmatrix}$$



$$[R][Z] = [V]$$

$$[R] = \begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix}$$

$$I = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}, \quad V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\left[\begin{array}{ccc} (R_1 + R_2 + R_3) & -R_2 & -R_3 \\ -R_2 & (R_2 + R_4 + R_5) & -R_5 \\ -R_3 & -R_5 & (R_3 + R_5 + R_6) \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ -V_3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} (R_1 + R_2 + R_3) & -R_2 & -R_3 \\ -R_2 & (R_2 + R_4 + R_5) & -R_5 \\ -R_3 & -R_5 & (R_3 + R_5 + R_6) \end{vmatrix} = \Delta$$


$$\Delta_1 = \begin{vmatrix} V_1 & -R_2 & -R_3 \\ V_2 & (R_2 + R_4 + R_5) & -R_5 \\ -V_3 & -R_5 & (R_3 + R_5 + R_6) \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} R_1 + R_2 + R_3 & -V_1 & -R_3 \\ -R_2 & V_2 & -R_5 \\ -R_3 & -V_3 & R_3 + R_5 + R_6 \end{vmatrix}$$

$$\Delta_3 = \begin{vmatrix} R_1 + R_2 + R_3 & -R_2 & V_1 \\ -R_2 & R_2 + R_4 + R_5 & V_2 \\ -R_3 & -R_5 & -V_3 \end{vmatrix}$$

$$[V] = [C] [A]$$

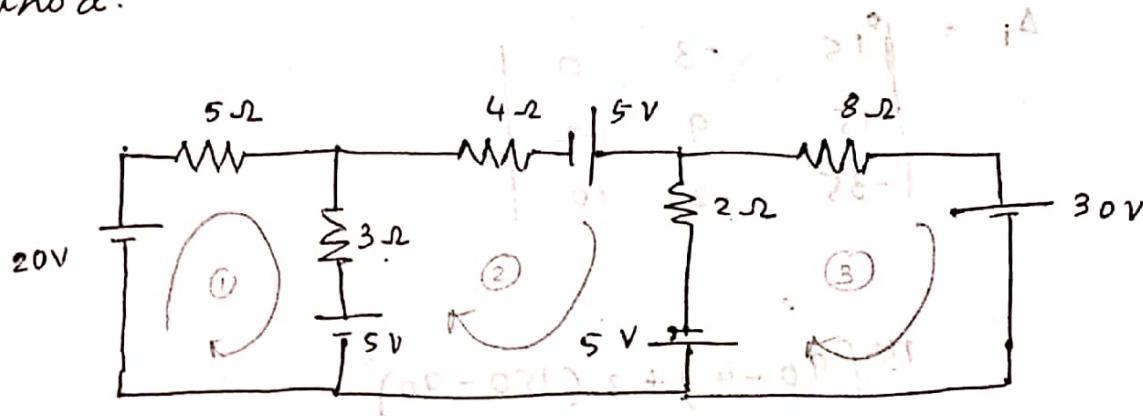* Find currents in each mesh using mesh current method.



$$\rightarrow [R][I] = [V]$$

$$R = \begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} = \begin{bmatrix} 5+3 & -3 & 0 \\ -3 & 3+4+2 & -2 \\ 0 & -2 & 2+8 \end{bmatrix}$$

$$I = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$V = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -5+20 \\ +5+5+5 \\ -30-5 \end{bmatrix}$$

$$\begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 15 \\ -35 \end{bmatrix}$$

$$B = \begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{bmatrix} = 8(90-4) + 3(-30+0) = 8 \times 86 - 90 = 598$$

$I_1 = \frac{\Delta_1}{\Delta}$. Area Area of Strands Half

$$\Delta_1 = \begin{vmatrix} 15 & -3 & 0 \\ 15 & 9 & -2 \\ -35 & 2 & 10 \end{vmatrix}$$

↓ ↓ ↓
V_{0.8} V_{0.8} V_{0.8}

$$= 15(90 - 4) + 3(150 - 70)$$

$$= 15 \times 86 + 3 \times 80$$

$$= 1530$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{1530}{598} = 2.5$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 8 & 15 & 0 \\ -3 & 9 & -2 \\ 0 & 2 & 10 \end{vmatrix}}{\begin{vmatrix} 8 & 15 & 0 \\ -3 & 9 & -2 \\ 0 & 2 & 10 \end{vmatrix}} = 2$$

$$\Delta_2 = \begin{vmatrix} 8 & 15 & 0 \\ -3 & 9 & -2 \\ 0 & 2 & 10 \end{vmatrix}$$

↓ ↓ ↓
V_{0.8} V_{0.8} V_{0.8}

$$= 8(90 + 4) - 15(-30 - 0)$$

$$= 8 \times 86 + 450$$

$$= 1138$$

$$I_2 = \frac{1138}{598} = 1.92$$

~~(1.92) $\times 4(1-0.8)$~~

$$= 0.96 \times 8 = 7.68$$

$$\Delta_3 = \begin{vmatrix} 8 & -3 & 15 \\ -3 & 9 & 9 \\ 0 & -2 & 2 \end{vmatrix}, \leftarrow \text{③ after } \rightarrow \text{②}$$

$$= 8(18 + 18) + 3(-6 + 0) + 15(6 + 0)$$

$$= -18 + 90$$

$$= 72$$


$$I_3 = \frac{72}{598} = 0.12$$

NODE VOLTAGE METHOD (Nodal Analysis)

This method is based on KCL

1. Identifying the nodes, one of the nodes can be taken as the reference node which is at ground potential.
2. if there are ' n ' no. of nodes then we have to solve $(n-1)$ equations.

Eg: Analysis with Voltage source

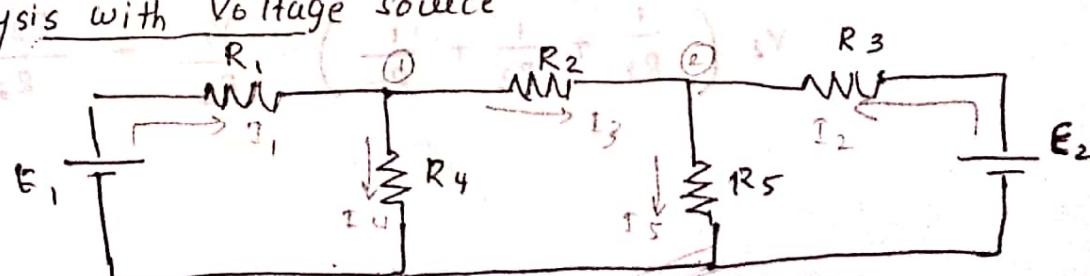

$n=3$

$n-1 = 3-2 = 2$ eqⁿ all need to solve.

$$KCL \text{ at node } ① \Rightarrow I_1 - I_3 - I_4 = 0$$

$$\left(\frac{E_1 - V_1}{R_1} \right) - \left(\frac{V_1 - V_2}{R_2} \right) - \frac{V_1}{R_4} = 0$$

$$\frac{E_1}{R_1} - \frac{V_1}{R_1} - \frac{V_1}{R_2} + \frac{V_2}{R_2} - \frac{V_1}{R_4} = 0$$

$$-V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) + \frac{V_2}{R_2} = -\frac{E_1}{R_1}$$

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) - \frac{V_2}{R_2} = \frac{E_1}{R_1} \quad ①$$

(2nd plan taban) node 2 satayee se

$$KCL \text{ at node } ② \Rightarrow I_3 + I_2 - I_5 = 0$$


top as band bottom side

$$\frac{V_1 - V_2}{R_2} + \frac{E_2 - V_2}{R_3} - \frac{V_2}{R_5} = 0$$

$$\frac{V_1}{R_2} - \frac{V_2}{R_2} + \frac{E_2}{R_3} - \frac{V_2}{R_3} - \frac{V_2}{R_5} = 0$$

$$-V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) + \frac{V_1}{R_2} = -\frac{E_2}{R_3}$$
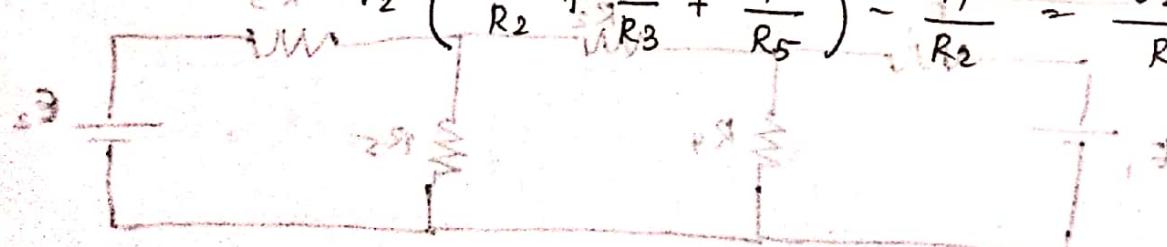
$$V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) - \frac{V_1}{R_2} = \frac{E_2}{R_3} \quad ②$$



From ① & ② =>


$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} E_1/R_1 \\ E_2/R_2 \end{bmatrix}$$

infinitesimal time step approach than set of linear
 $V_1 = \Delta_1/\Delta$

shorten with not desired form of answer set
 $V_2 = \Delta_2/\Delta$

$$\Delta = \begin{vmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) \end{vmatrix}$$

Analysis with current sources

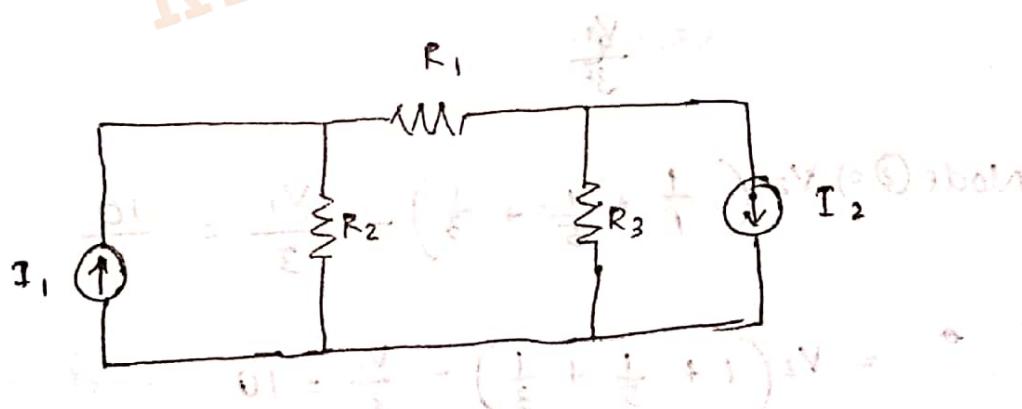


$$\text{Node ①} \Rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_2}{R_1} = I_1$$

$$\text{Node ②} \Rightarrow V_2 \left(\frac{1}{R_1} + \frac{1}{R_3} \right) - \frac{V_1}{R_1} = I_2$$

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} \right) & -\frac{1}{R_1} \\ -\frac{1}{R_1} & \left(\frac{1}{R_1} + \frac{1}{R_3} \right) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

(Q)

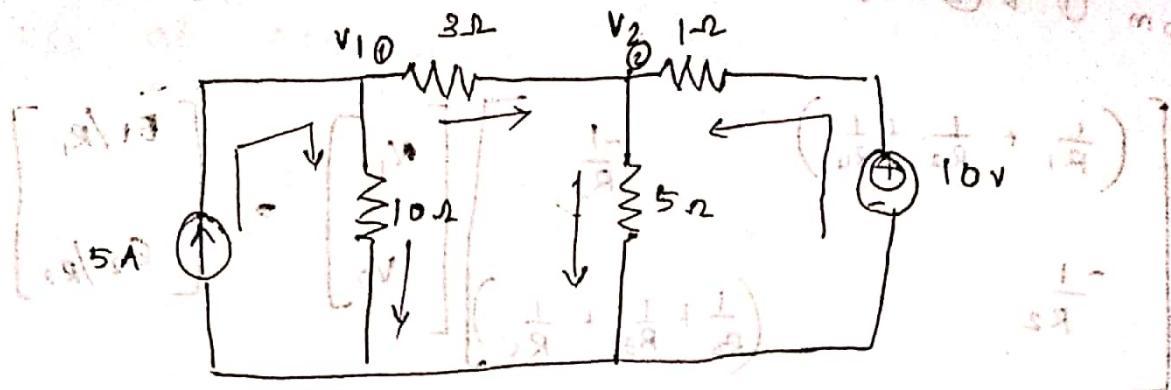

Write the node voltage eq^{n's} and determine the current in each branch for the network shown.

→

$$\text{Node } \textcircled{1} \Rightarrow V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_2}{R_1} = I_1$$

$$V_1 \left(\frac{1}{3} + \frac{1}{10} \right) - \frac{V_2}{3} = 5$$

$$= \frac{V_1}{3}$$

$$\text{Node } \textcircled{2} \Rightarrow V_2 \left(\frac{1}{1} + \frac{1}{5} + \frac{1}{3} \right) - \frac{V_1}{3} = \frac{10}{1}$$

$$= V_2 \left(1 + \frac{1}{5} + \frac{1}{3} \right) - \frac{V_1}{3} = 10$$

$$I = \frac{V_1}{3} = \left(\frac{1}{3} + \frac{1}{10} \right) V \quad \leftarrow \textcircled{1} \text{ solve}$$

$$= V_2 \frac{23}{15} \quad \leftarrow \frac{V_1}{3} = \left(\frac{1}{3} + \frac{1}{10} \right) V \quad \leftarrow \textcircled{2} \text{ solve}$$

$$\begin{bmatrix} \frac{1}{10} & \frac{-1}{3} \\ \frac{-1}{3} & \frac{23}{15} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$

$$\frac{23}{15} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$

$\Delta = 0.05633 = \frac{83}{150}$

$$\Delta_1 = \begin{vmatrix} 5 & -V_3 \\ 10 & 23/15 \end{vmatrix} = 11$$

notation: V_3 is the third branch

$$\Delta_2 = \begin{vmatrix} 13/30 & 5 \\ -V_3 & 10 \end{vmatrix} = 6$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{11}{83/150} = \frac{11}{0.55} = \underline{\underline{19.87 \text{ V}}}$$

$$V_2 = \frac{6}{0.55} = \underline{\underline{10.9 \text{ V}}}$$


$$I_1 = \frac{V_1}{10} = \frac{19.87}{10} = \underline{\underline{1.987 \text{ A}}}$$

$$I_2 = \frac{V_1 - V_2}{3} = \frac{19.87 - 10.84}{3} = \underline{\underline{3.01 \text{ A}}}$$


$$I_3 = \frac{V_2 - 0}{5} = \frac{10.84}{5} = \underline{\underline{2.168 \text{ A}}}$$

$$I_4 = \frac{10 - V_2}{10} = \frac{10 - 10.84}{10} = \underline{\underline{-0.084 \text{ A}}}$$
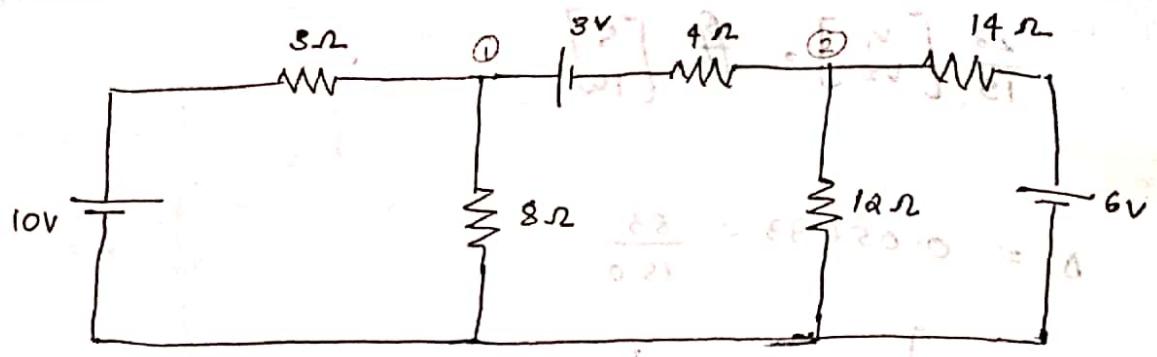
$$\begin{bmatrix} 0 \\ 1 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$



Find current through 8Ω & 12Ω resistor.

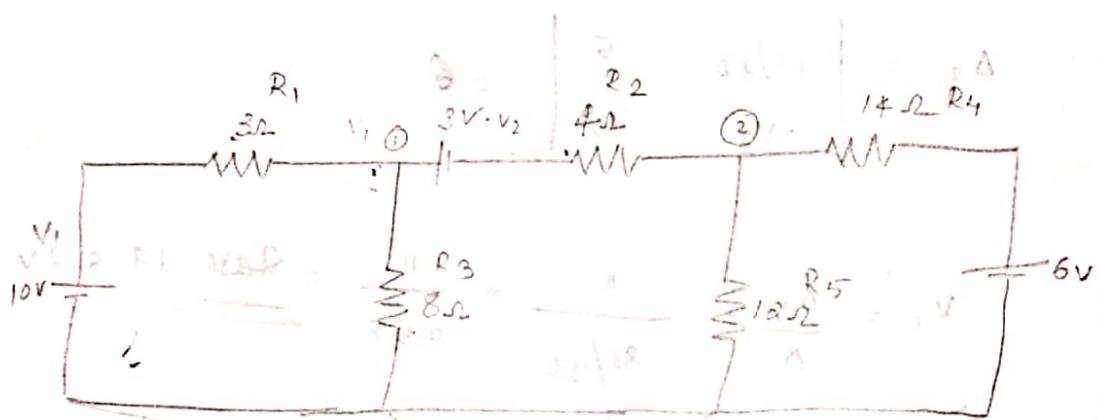

$$n = 3$$

$$n-1 = 3-2 = 1 \text{ eqn}$$

$$\text{Node } ① \Rightarrow V_1 \left(\frac{1}{3} + \frac{1}{8} + \frac{1}{4} \right) - \frac{V_2}{4} = \frac{10}{3}$$

$$\text{Node } ② \Rightarrow V_2 \left(\frac{1}{4} + \frac{1}{12} + \frac{1}{4} \right) - \frac{V_1}{4} = \frac{6}{12}$$

$$\begin{bmatrix} \frac{1}{3} + \frac{1}{8} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{12} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{10}{3} \\ \frac{6}{12} \end{bmatrix}$$

$$\begin{bmatrix} 0.708 & -0.25 \\ -0.25 & 0.404 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3.33 + \frac{3}{4} \\ 0.42 - \frac{3}{4} \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.708 & -0.25 \\ -0.25 & 0.404 \end{vmatrix} = \begin{vmatrix} 17/24 & -1/4 \\ -1/4 & 17/42 \\ 0.404 & \end{vmatrix}$$

$$= \frac{47}{386} = 0.224$$

$$\Delta_1 = \begin{vmatrix} 0.708 & -0.25 \\ 3.33 + \frac{3}{4} & 17/42 \\ 0.42 - \frac{3}{4} & \end{vmatrix}$$

$$\text{Ans } \frac{0.793}{0.224} = 1.57$$

$$(4.08 \times 0.404) - (-0.25 + 0.33)$$

$$= 1.988 = 0.09952$$

$$\Delta_2 = \begin{vmatrix} 17/24 & 10/3 + \frac{3}{4} \\ -1/4 & 6/14 - \frac{3}{4} \end{vmatrix} = \frac{1585}{1668} = 0.957 \frac{533}{672} = 0.7$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{0.793}{0.224} = 3.57$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{1.57}{0.224} = 11.22$$

$$I_1 = \underline{V_1}$$


$$V_1 = \frac{1.57}{0.139} = 7.01$$

$$V_2 = \frac{0.793}{0.139} = 5.71 V$$

$$I_1 = \frac{V_1}{R_1} = \frac{2.8}{8} = 0.35 A$$

$$I_2 = \frac{V_2}{R_2} = \frac{3.54}{12} = 0.294 A$$

Q Find power in each resistor

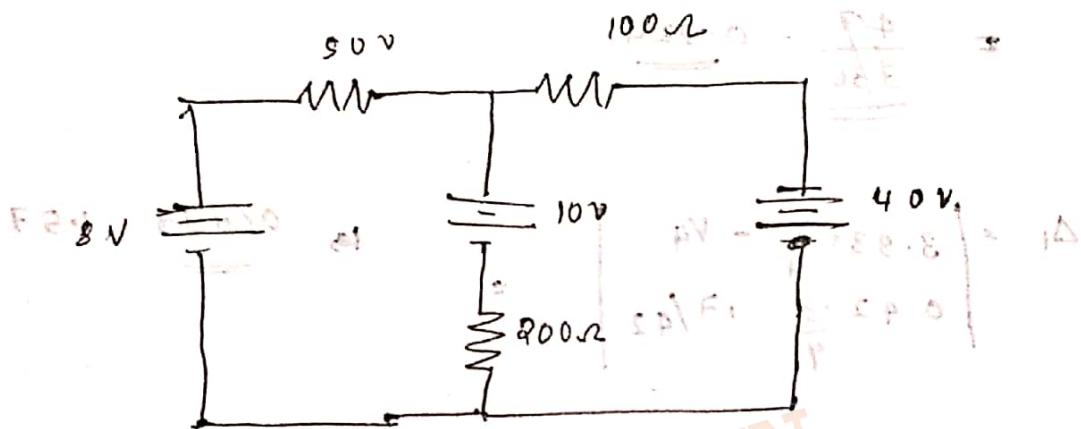

$$\frac{2.8}{10} = \frac{EPF}{10} = \frac{1A}{10} = 0.2 A$$

$$2.8 = \frac{EPF}{10} = \frac{50}{10} = 5 V$$

$$V = 5 V$$

$$10 \cdot F = \frac{EPF}{10} = 1 V$$

$$V \cdot A \cdot S = \frac{EPF}{10} = 1 V$$

Scan to enter site
www.ktunotes.in

Get it on play store
bit.ly/ktunotesapp



KTUnotes
The learning companion.